

Bipolar Junction Transistor (BJT)



Module:3	Transistors	5 hours
Bipolar Junction Transistor (BJT) - Device structure and physical operation, Concept of CB, CE and CC Configuration, Transistor as a Switch, - Metal-Oxide Field Effect Transistor (MOSFET) - Device Structure, Mode of operation and Characteristics, MOSFET configurations (CS, CD and CG).		

<https://www.youtube.com/watch?v=-VwPSDQmdjM>

Bipolar Junction Transistor (BJT)



Bipolar Junction Transistor (BJT)

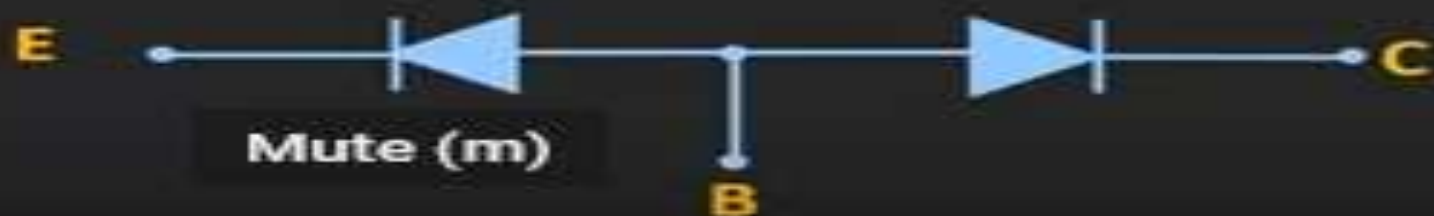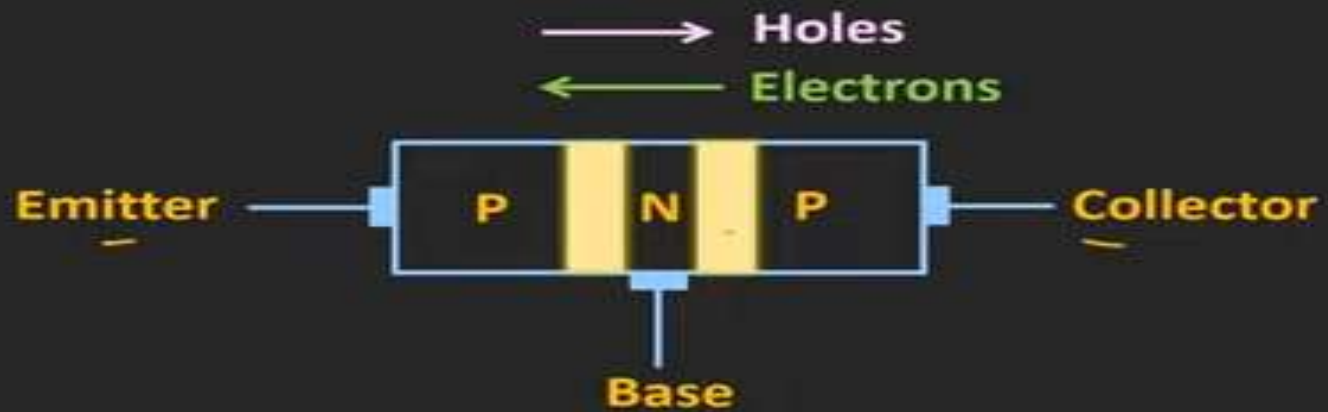

Bipolar Junction Transistor (BJT)



Emitter	Heavily Doped
Base	Lightly Doped
Collector	Moderately Doped

Base - Very Thin

Different Regions of Operation

Active Region


Cut-off Region

Saturation Region

Bipolar Junction Transistor (BJT)


Different Regions of Operation

Active Region

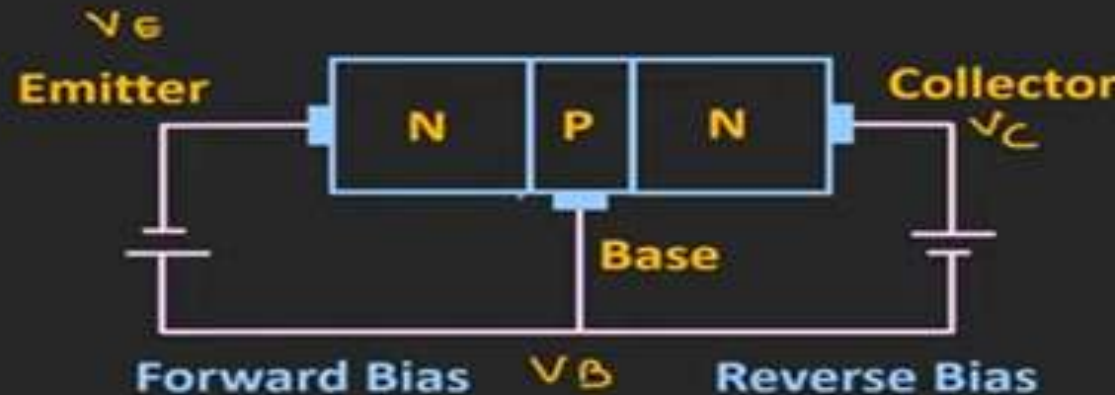

Different Regions of Operation

Active Region

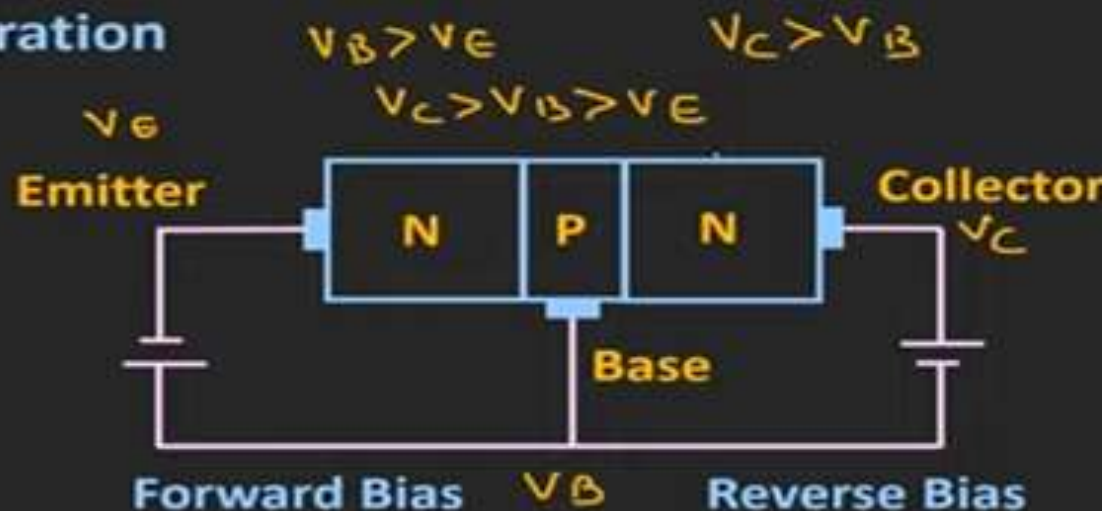


Bipolar Junction Transistor (BJT)

Different Regions of Operation

$$V_E > V_B \quad V_C > V_B$$

Cut-off Region

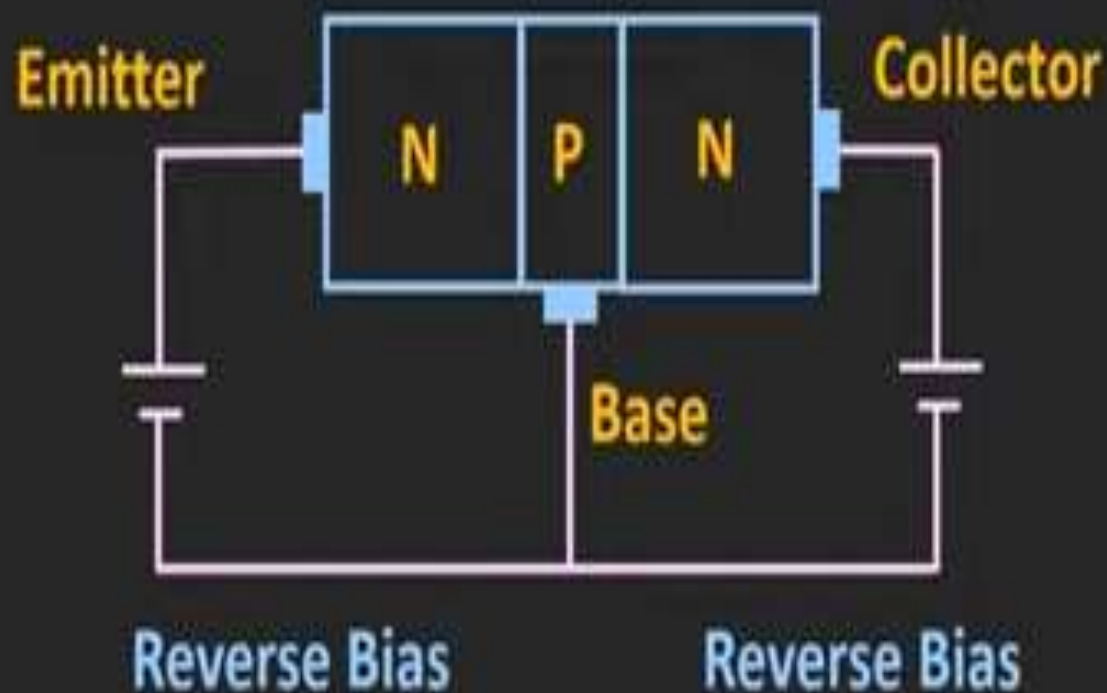


Bipolar Junction Transistor (BJT)

Different Regions of Operation

$$V_B > V_E$$

$$V_B > V_C$$

Saturation Region

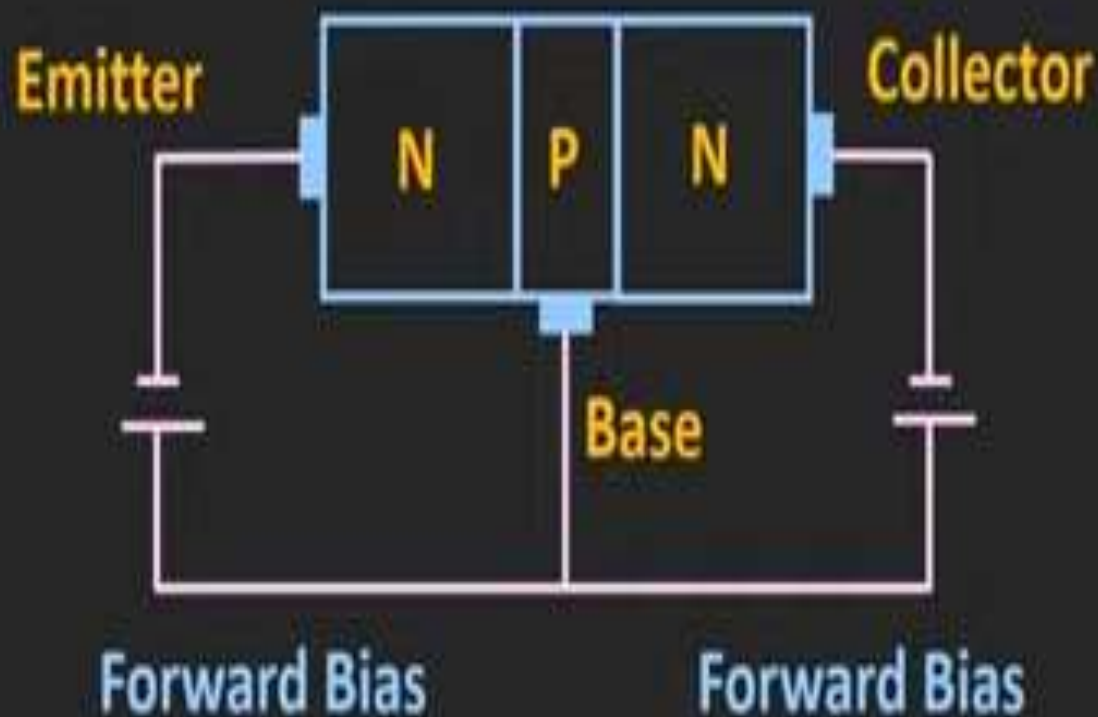

Bipolar Junction Transistor (BJT)


Different Regions of Operation

$$V_E > V_B$$

$$V_B > V_C$$

Active Region

$$V_E > V_B > V_C$$

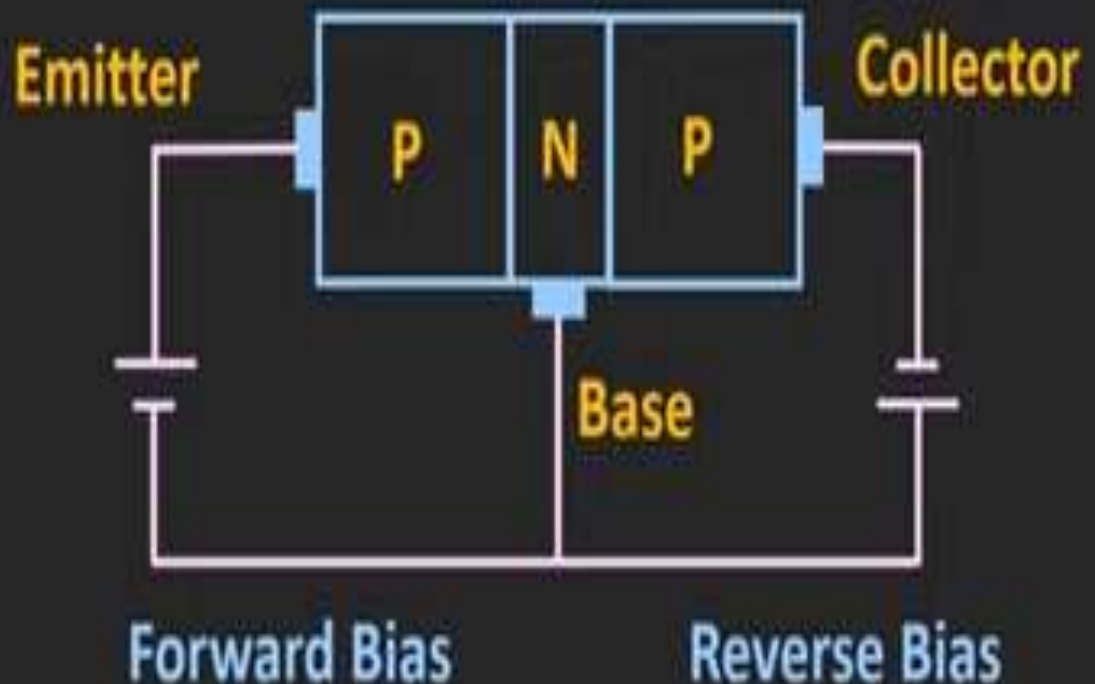

Bipolar Junction Transistor (BJT)

Different Regions of Operation


Active Region Amplification

Cut-off Region Switching



Saturation Region

Bipolar Junction Transistor (BJT)

Symbol

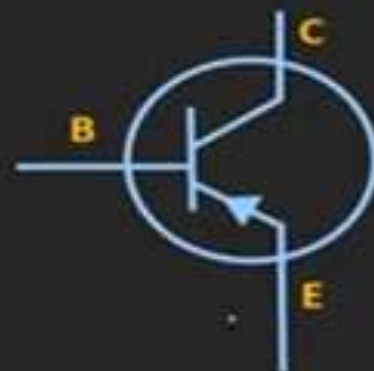


Symbol

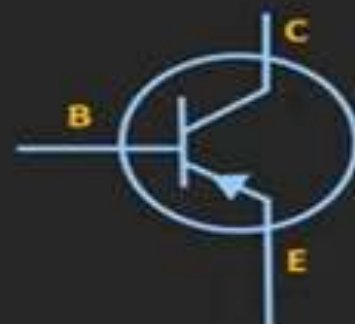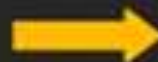


Bipolar Junction Transistor (BJT)

BJT Configuration


Common Emitter

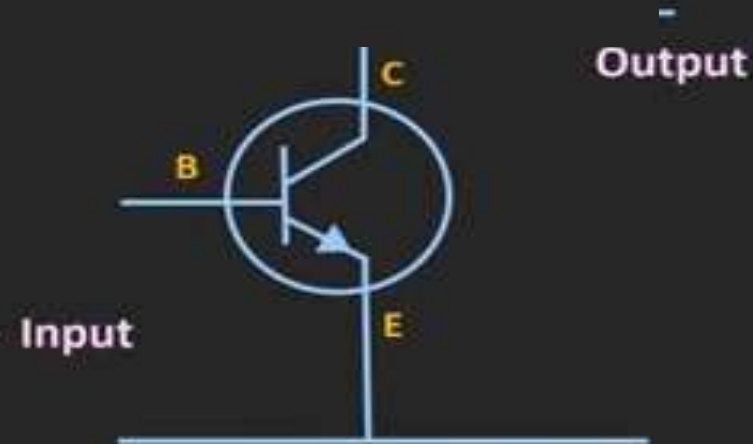


Common Collector

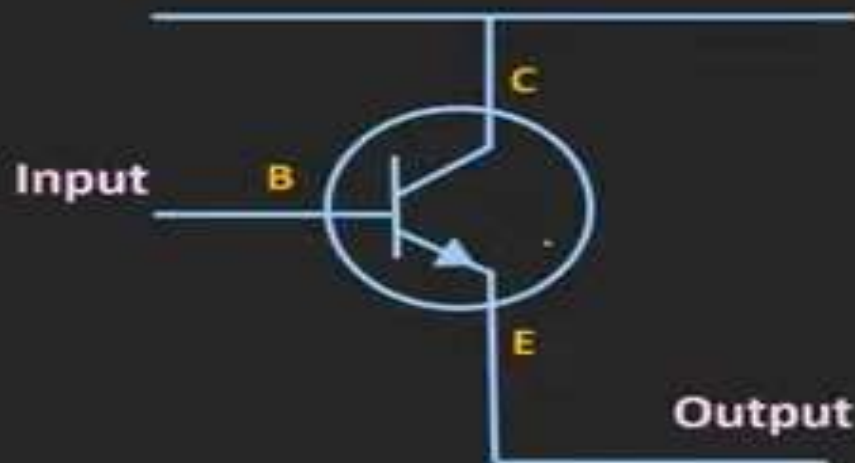

Common Base

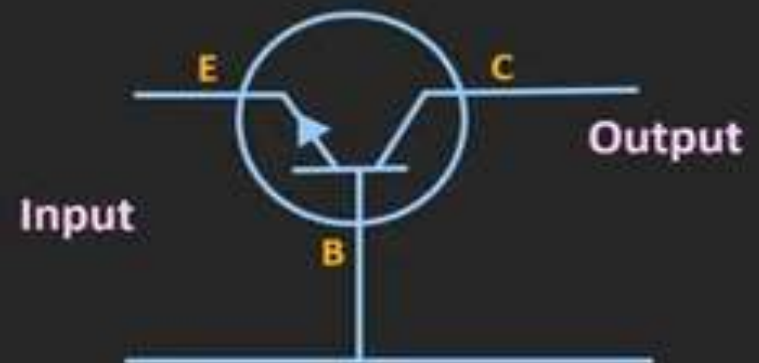


Working of BJT

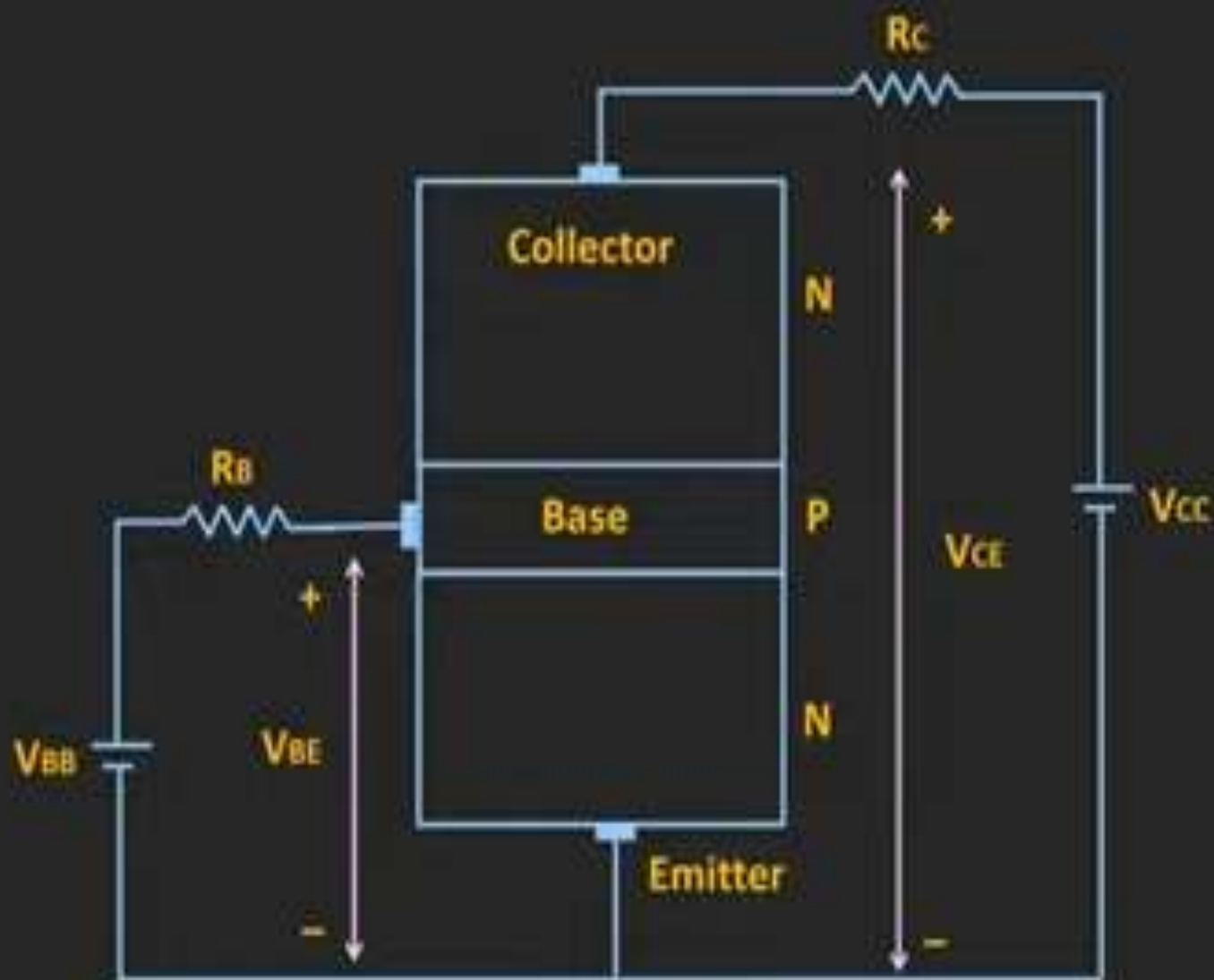

Working of BJT

$$V_{BE} \sim 0.7V$$

$$V_{CB}$$

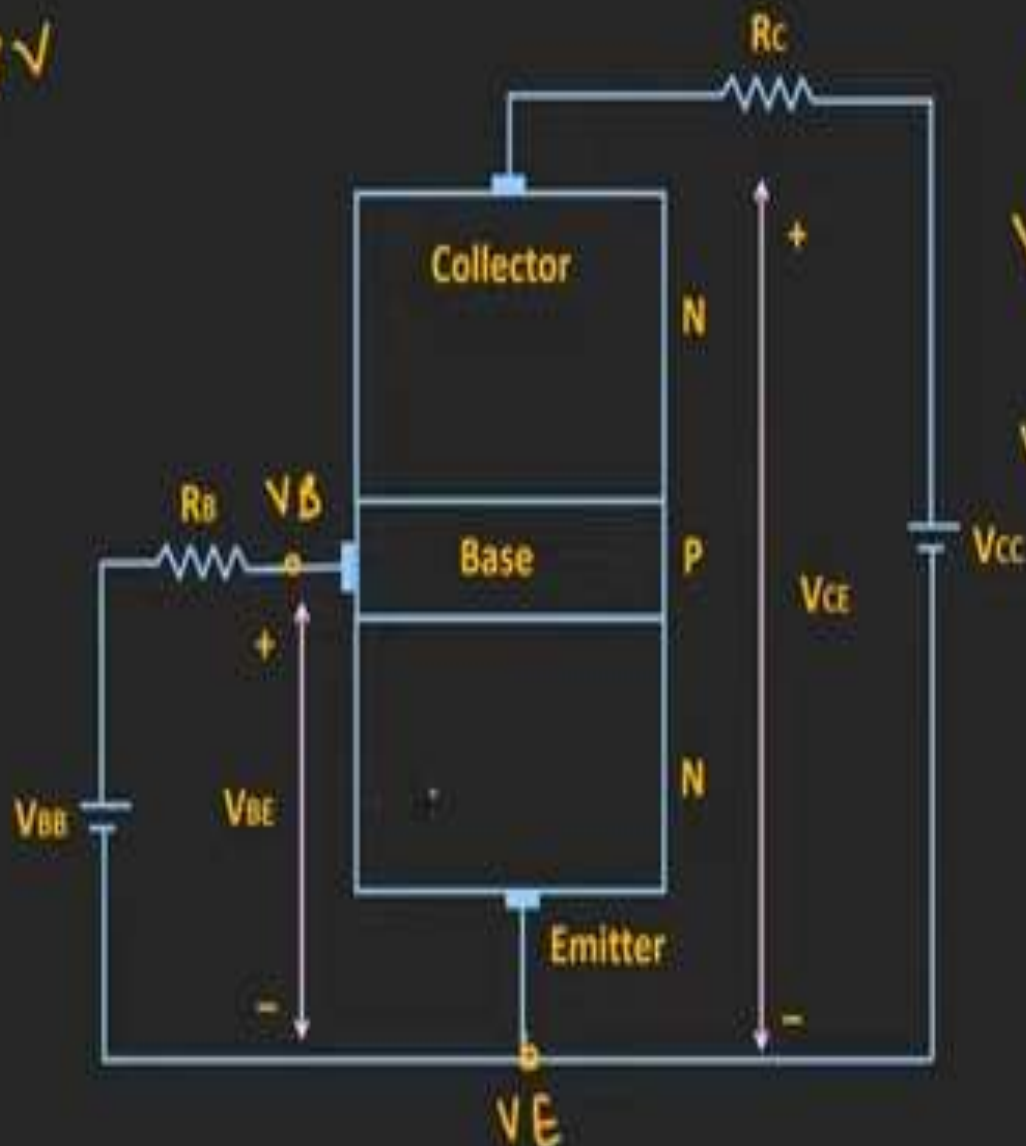


$$V_{BE} = V_B - V_E$$

$$V_{CE} = V_C - V_E$$


$$V_{EB} = V_E - V_B \\ = -V_{BE}$$




Working of BJT

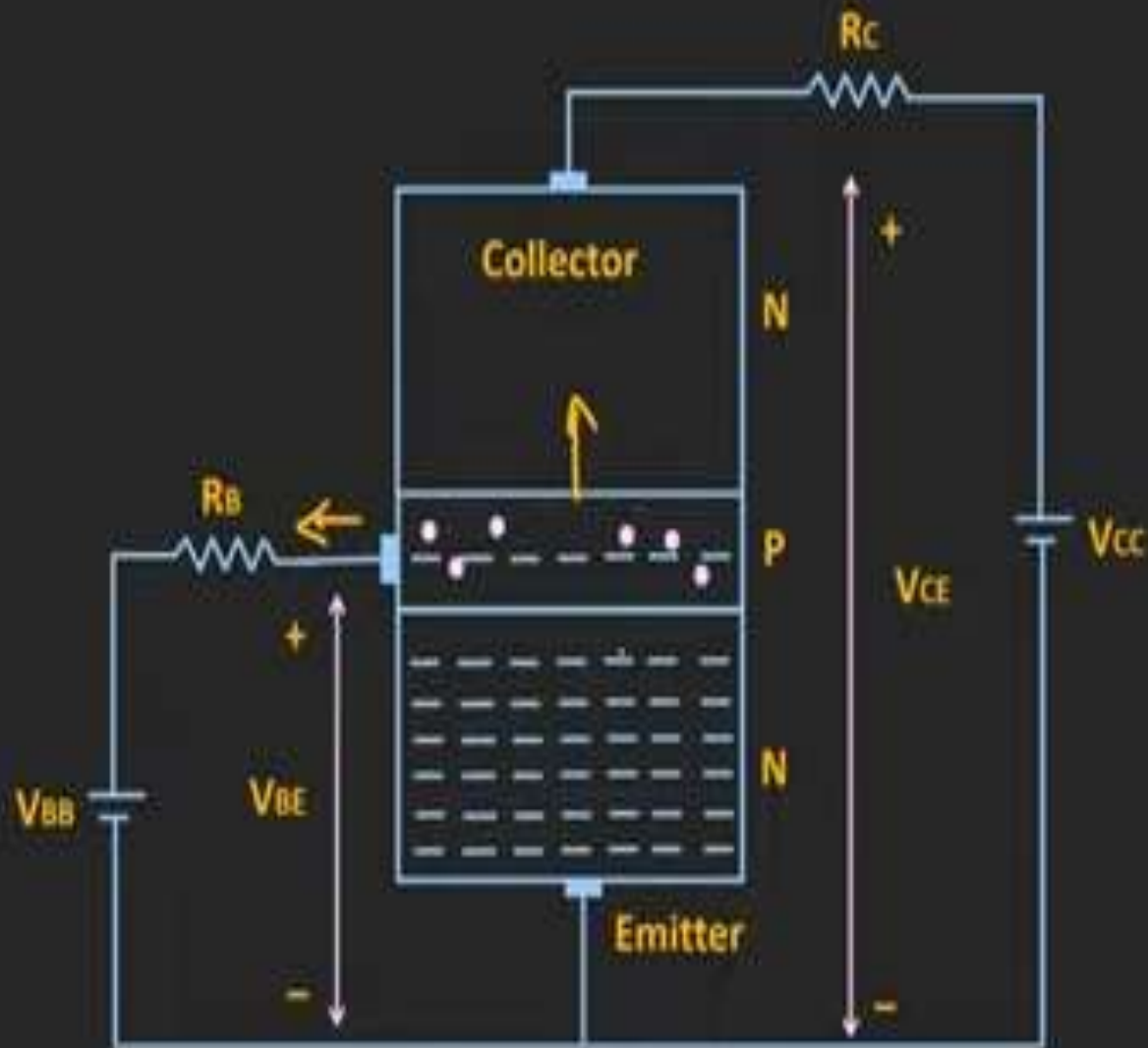


Working of BJT

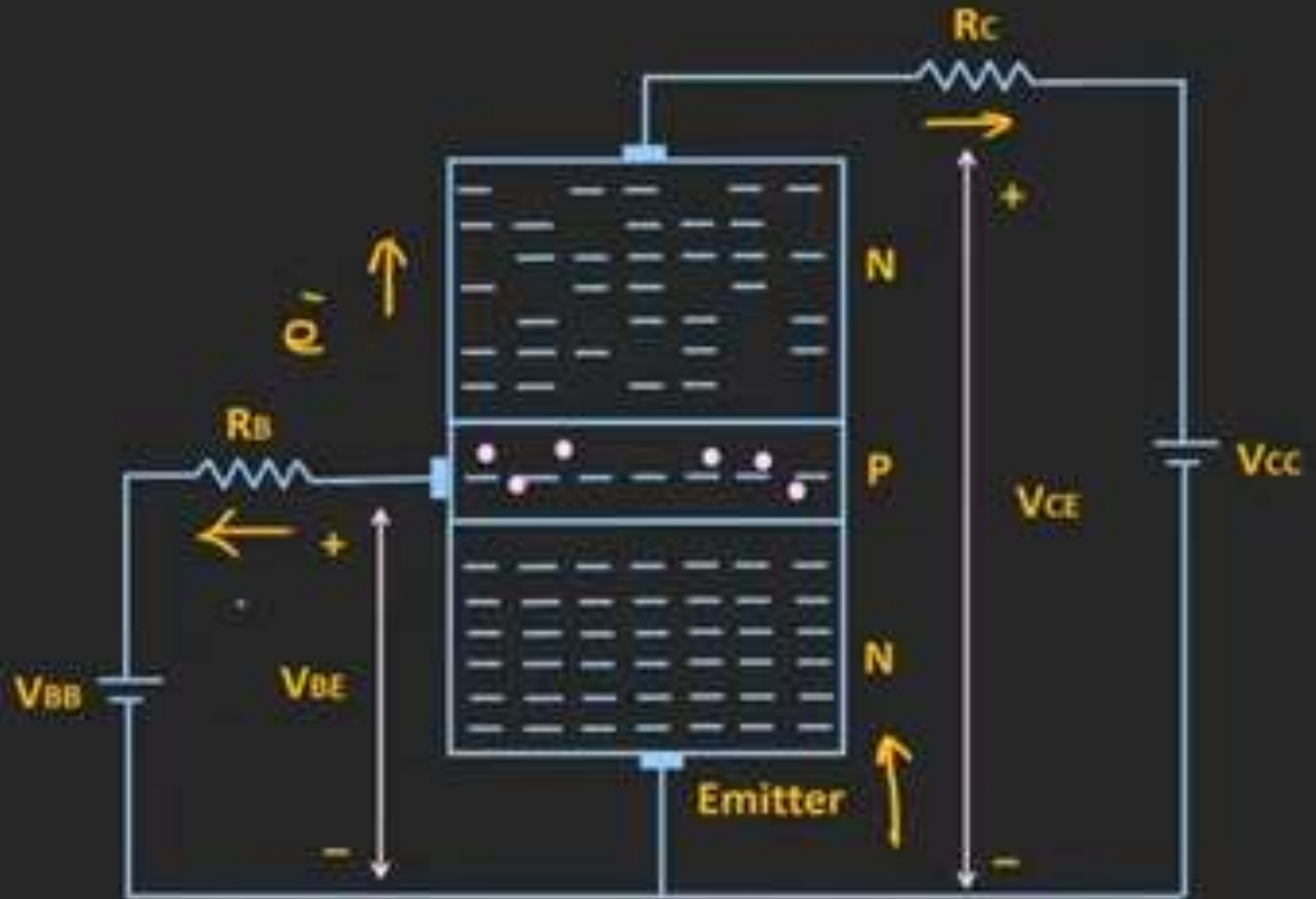

Current in BJT

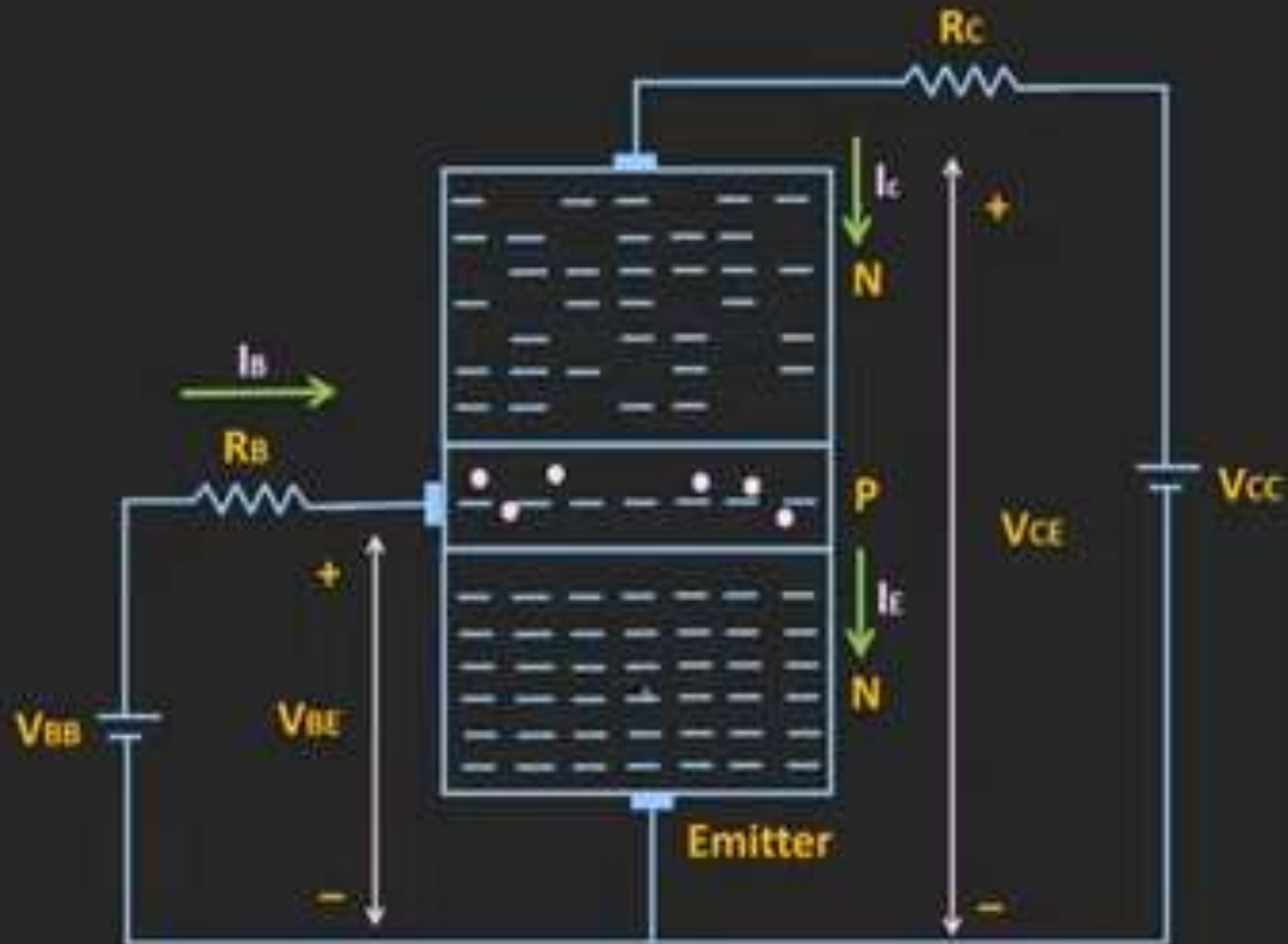

Current in BJT

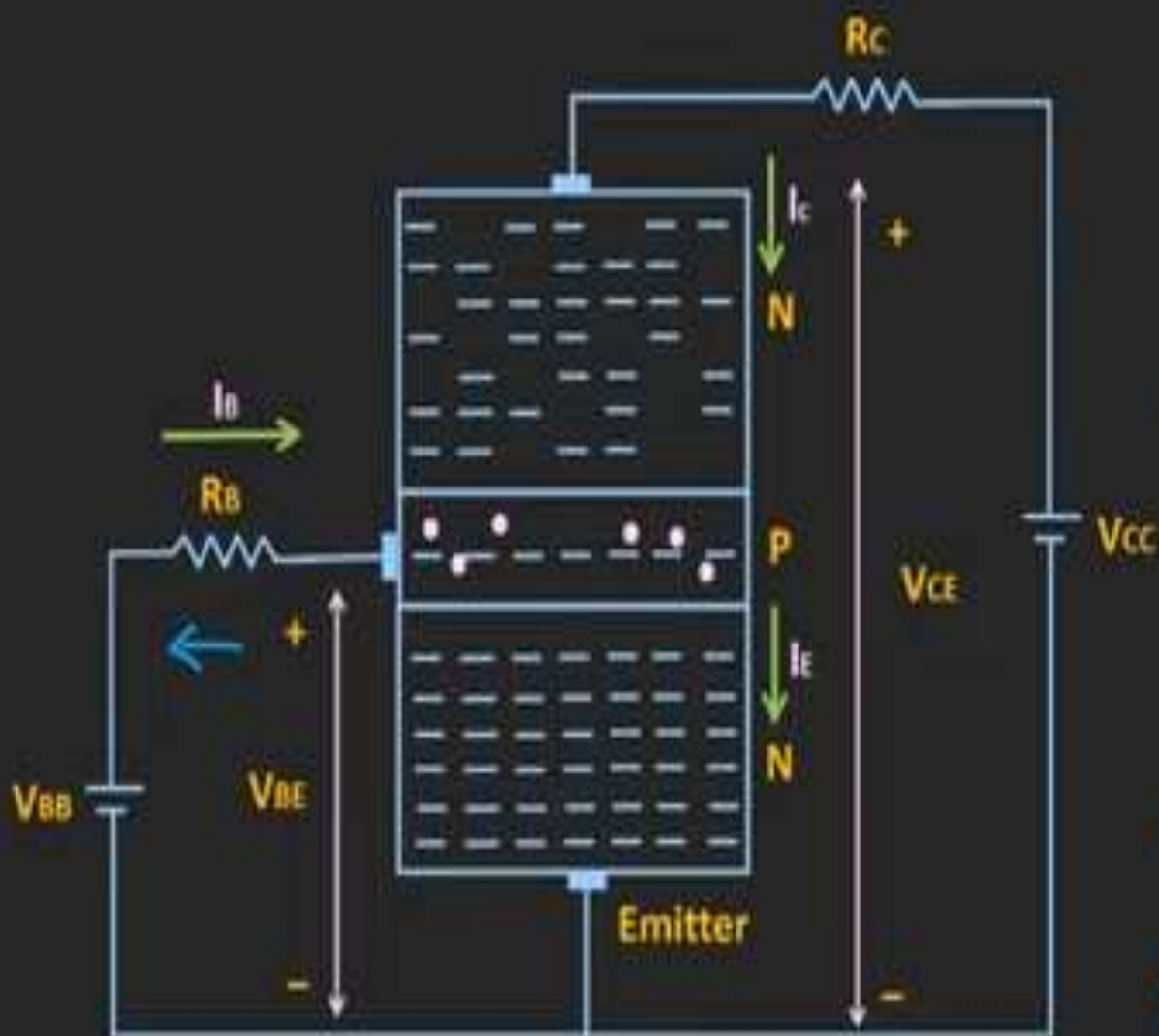

$$I_B + I_C = I_E$$

$$I_C \approx I_E$$


$$\Rightarrow I_C = \alpha I_E$$

$$I_B + \alpha I_E = I_E$$

$$\Rightarrow I_B = (1 - \alpha) I_E$$

$$\Rightarrow I_B = (1 - \alpha) \times \frac{I_C}{\alpha}$$

Current in BJT

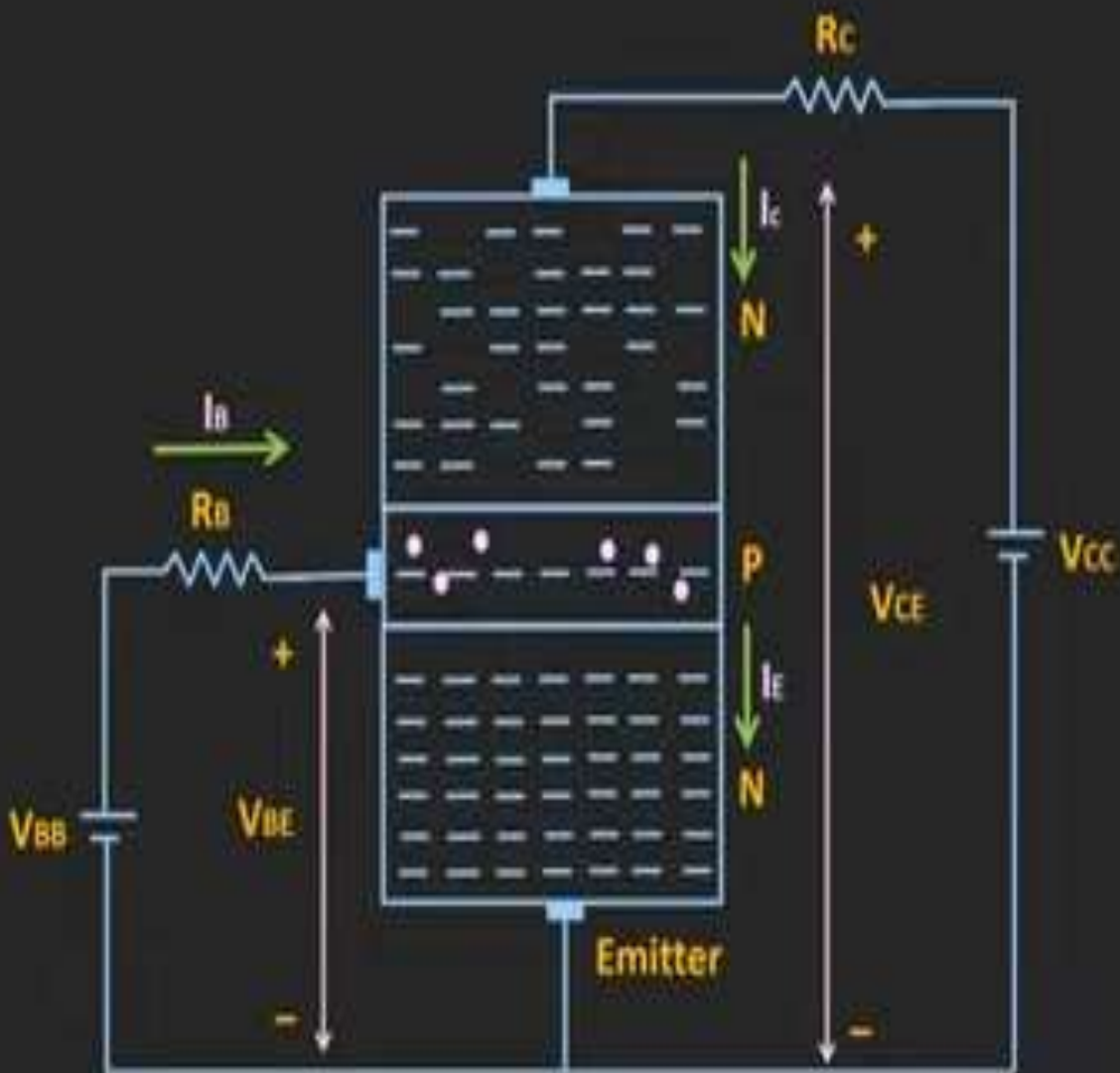

$$I_B = \frac{1 - \alpha}{\alpha} \times I_C$$

$$\Rightarrow I_C = \frac{\alpha}{\frac{1 - \alpha}{\beta}} \times I_B$$


$$\Rightarrow I_C = \beta I_B$$

BJT


Common Emitter Configuration

<https://www.youtube.com/watch?v=KynKHr2cXgk>

Common Emitter (CE) Configuration

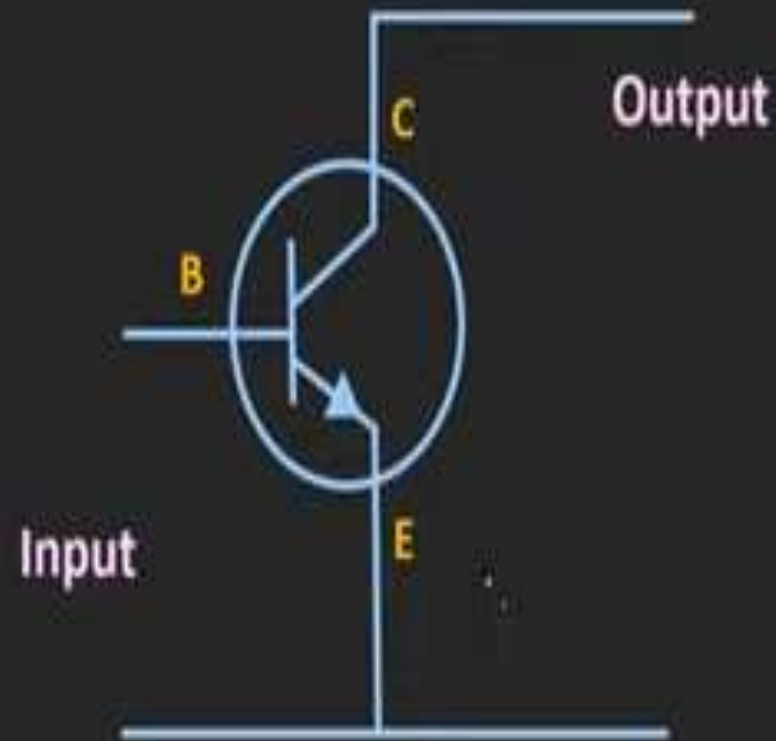

Common Emitter (CE) Configuration

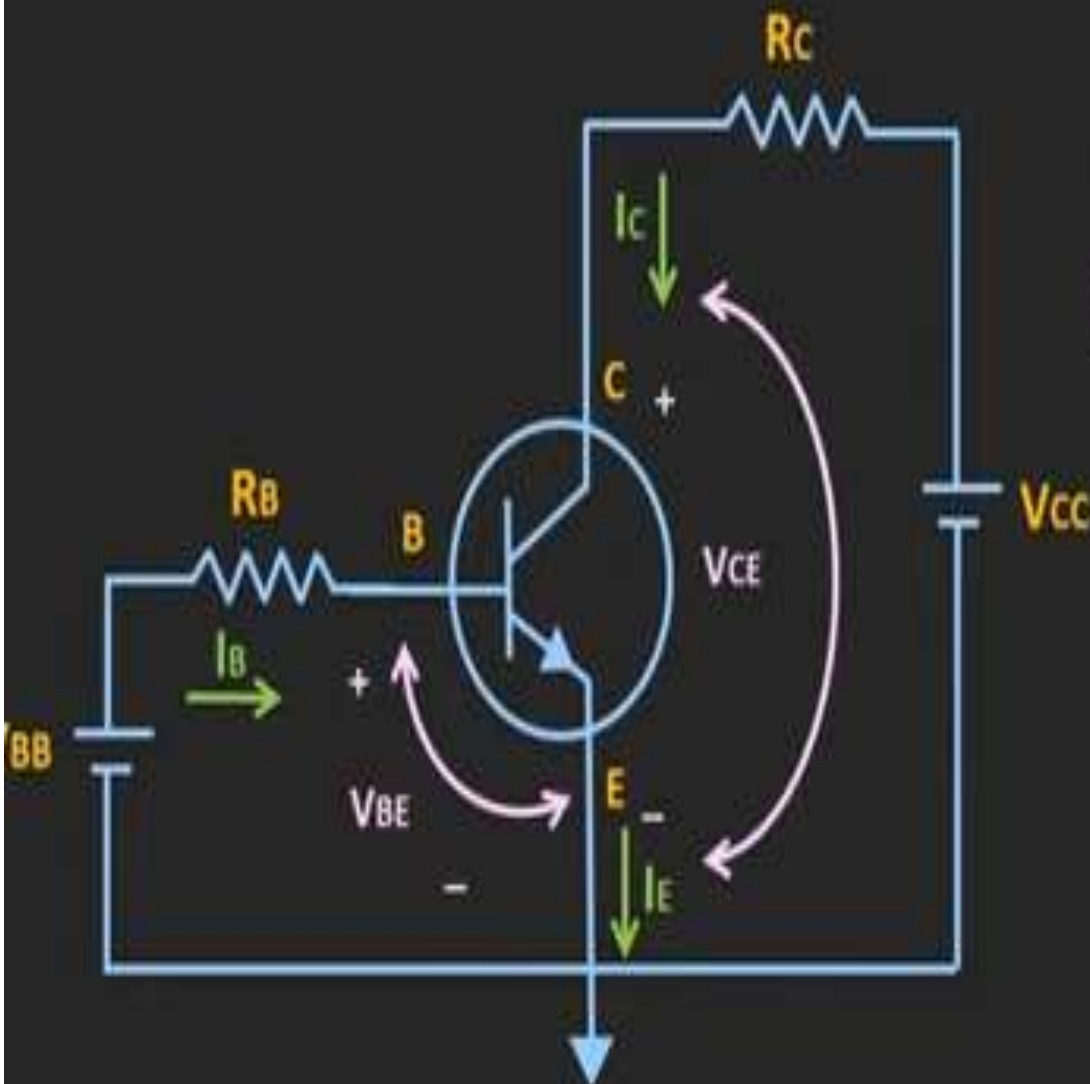

Base- Emitter Junction - Forward Bias


Collector- Base Junction - Reverse Bias

I_B

I_C




Common Emitter (CE) Configuration

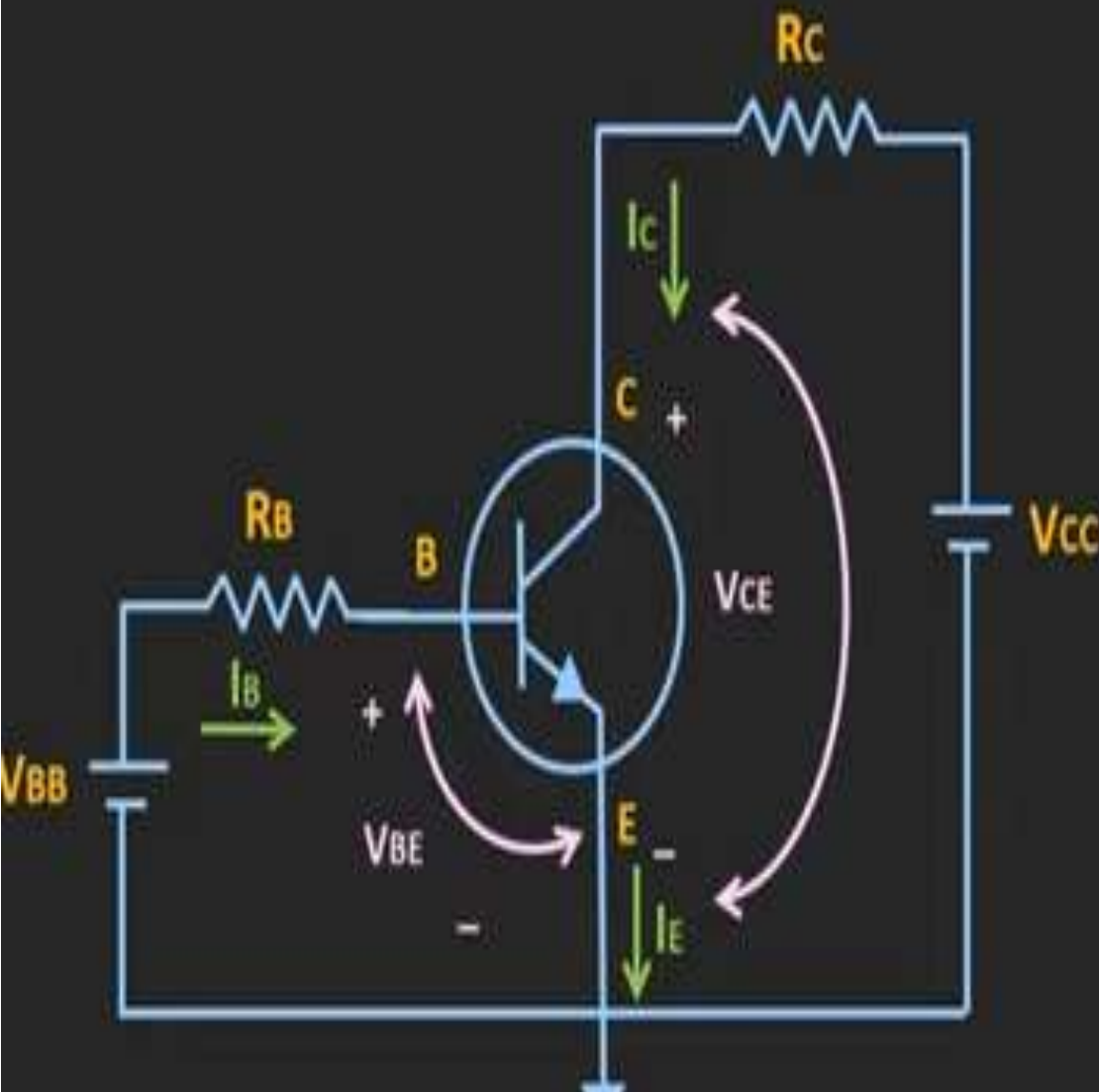


Base- Emitter Junction - Forward Bias

Collector- Base Junction - Reverse Bias

Common Emitter (CE) Configuration

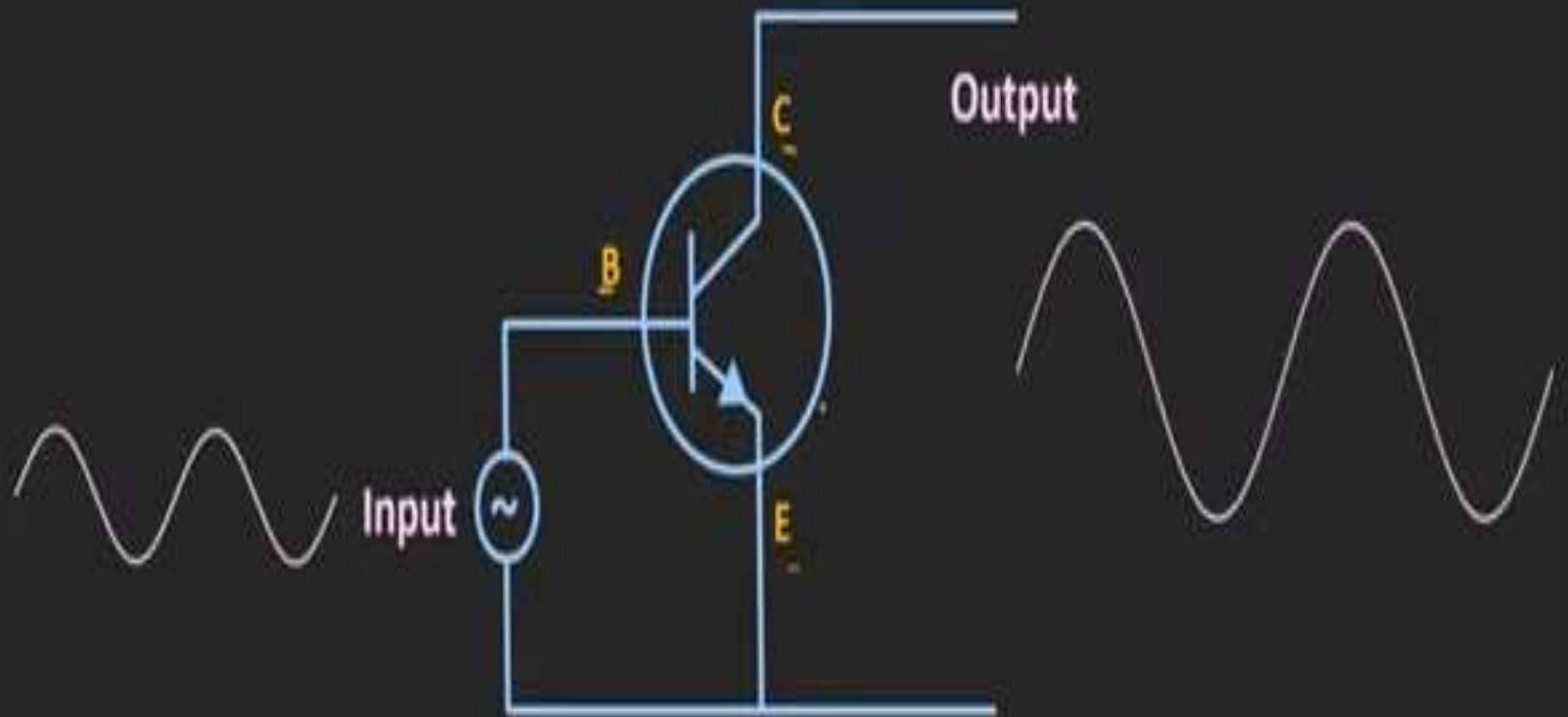

Common Emitter (CE) Configuration

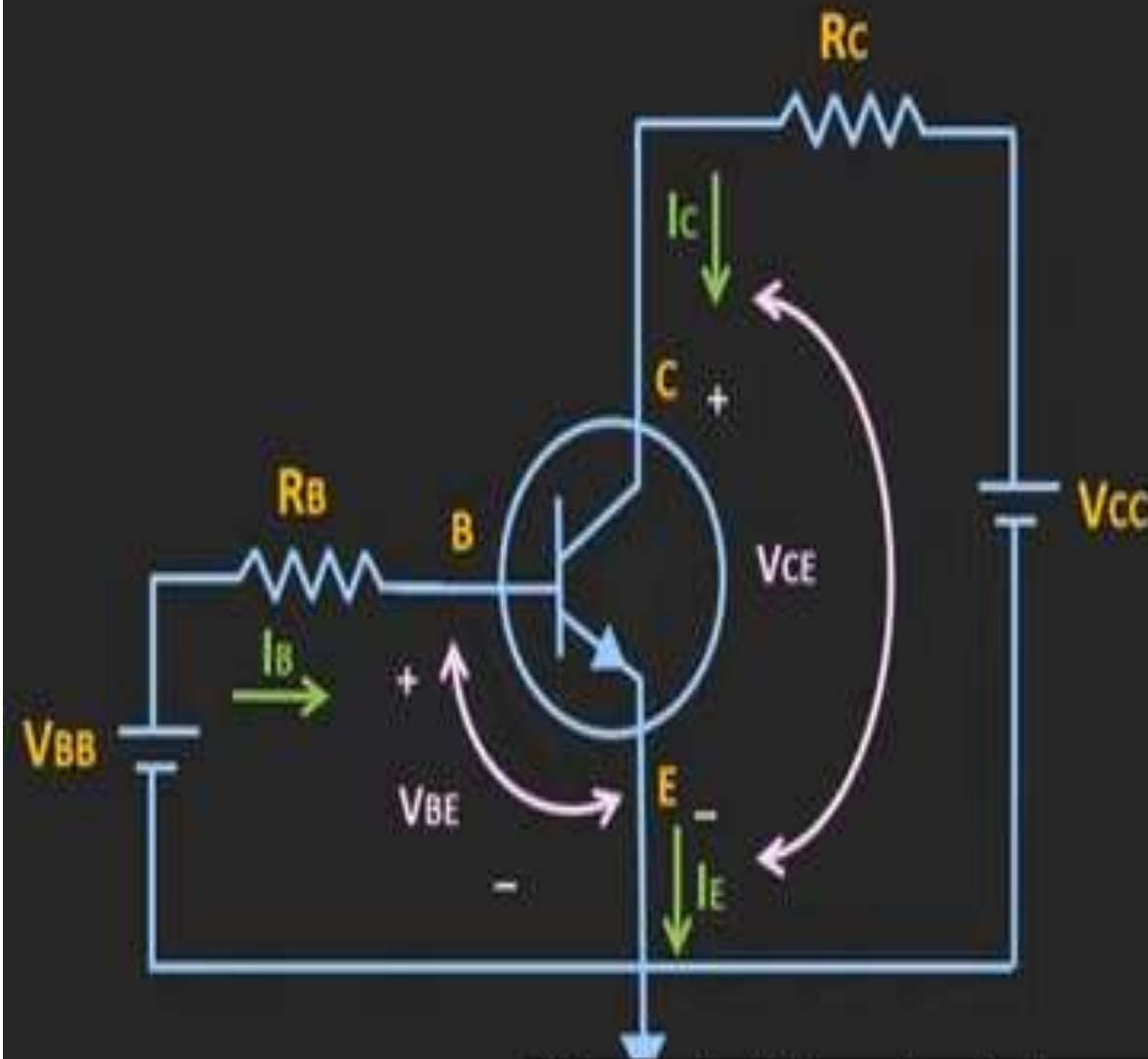

Input Characteristics

V_{BE} , I_B


Output Characteristics

V_{CE} , I_C


Similarly, this output characteristic defines

Common Emitter (CE) Configuration

Input Characteristics

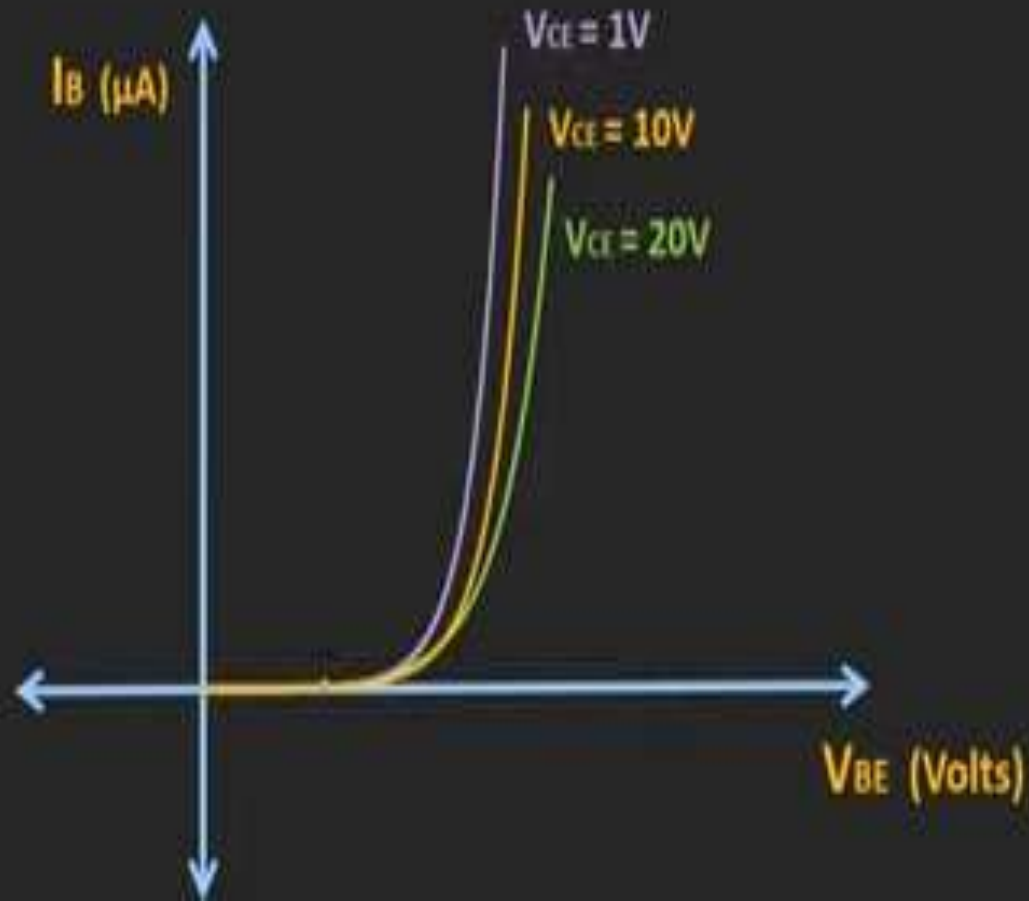


Common Emitter (CE) Configuration

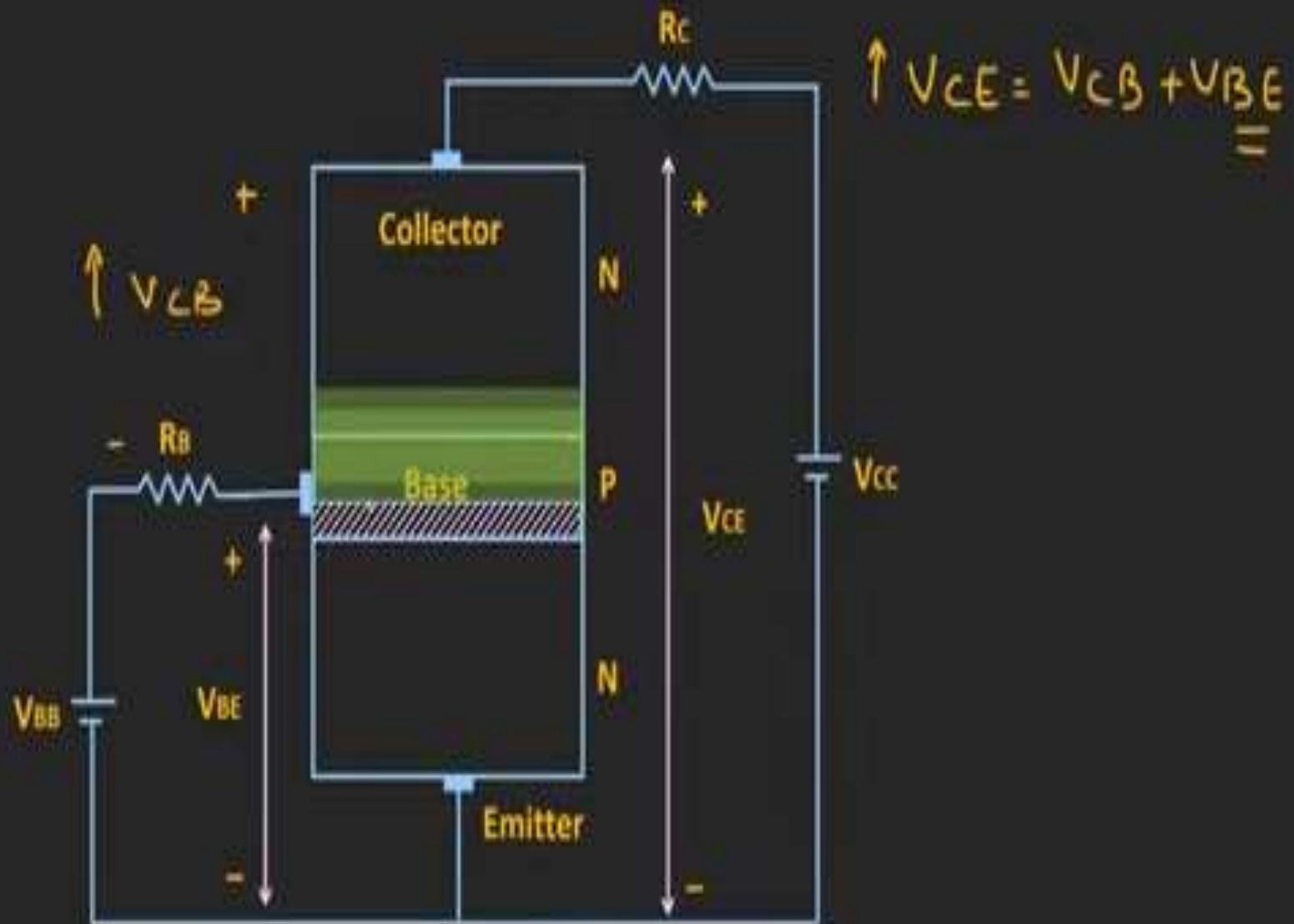

Common Emitter (CE) Configuration


Output Characteristics

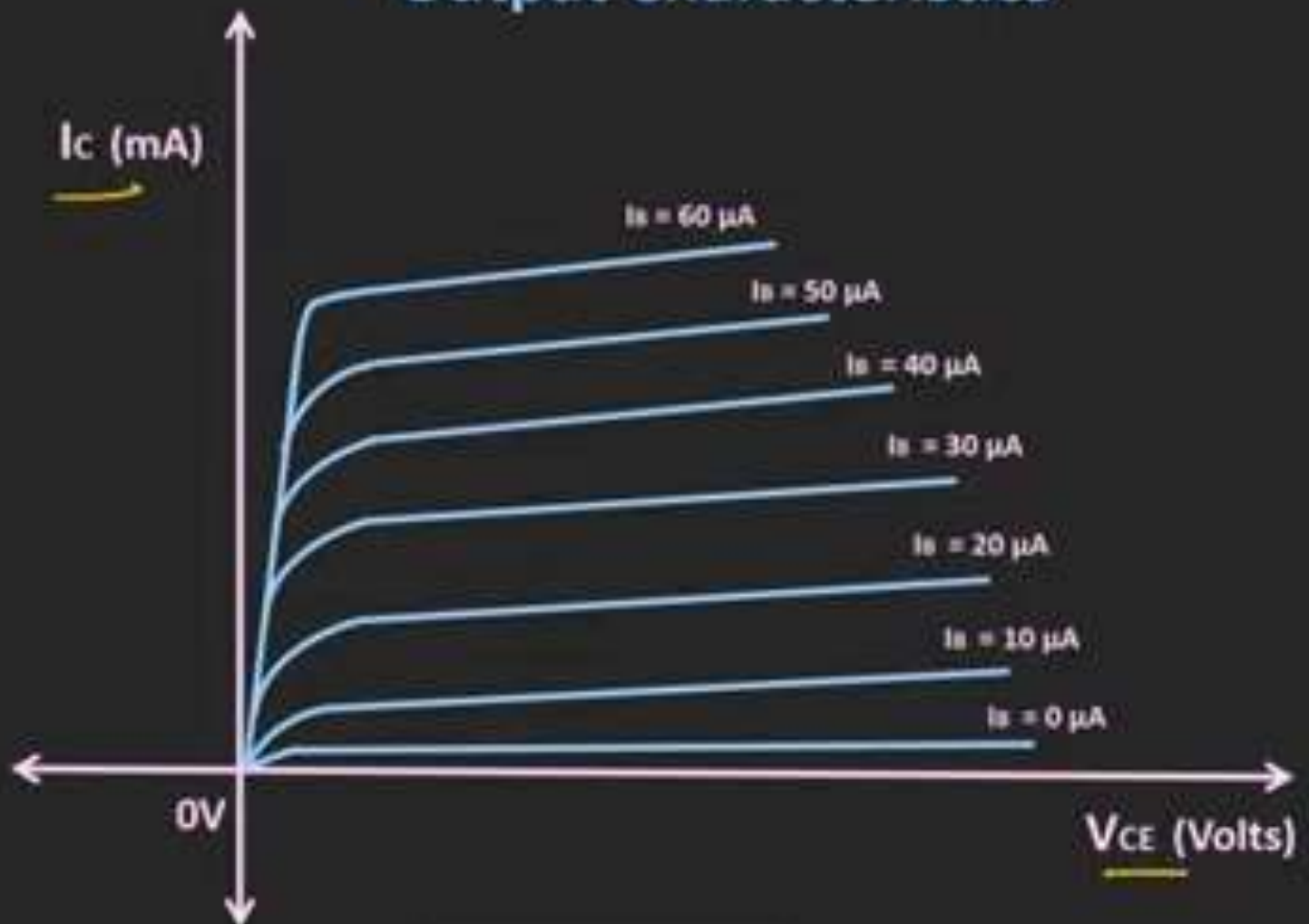

voltage V_{ce} .

Common Emitter (CE) Configuration

Output Characteristics

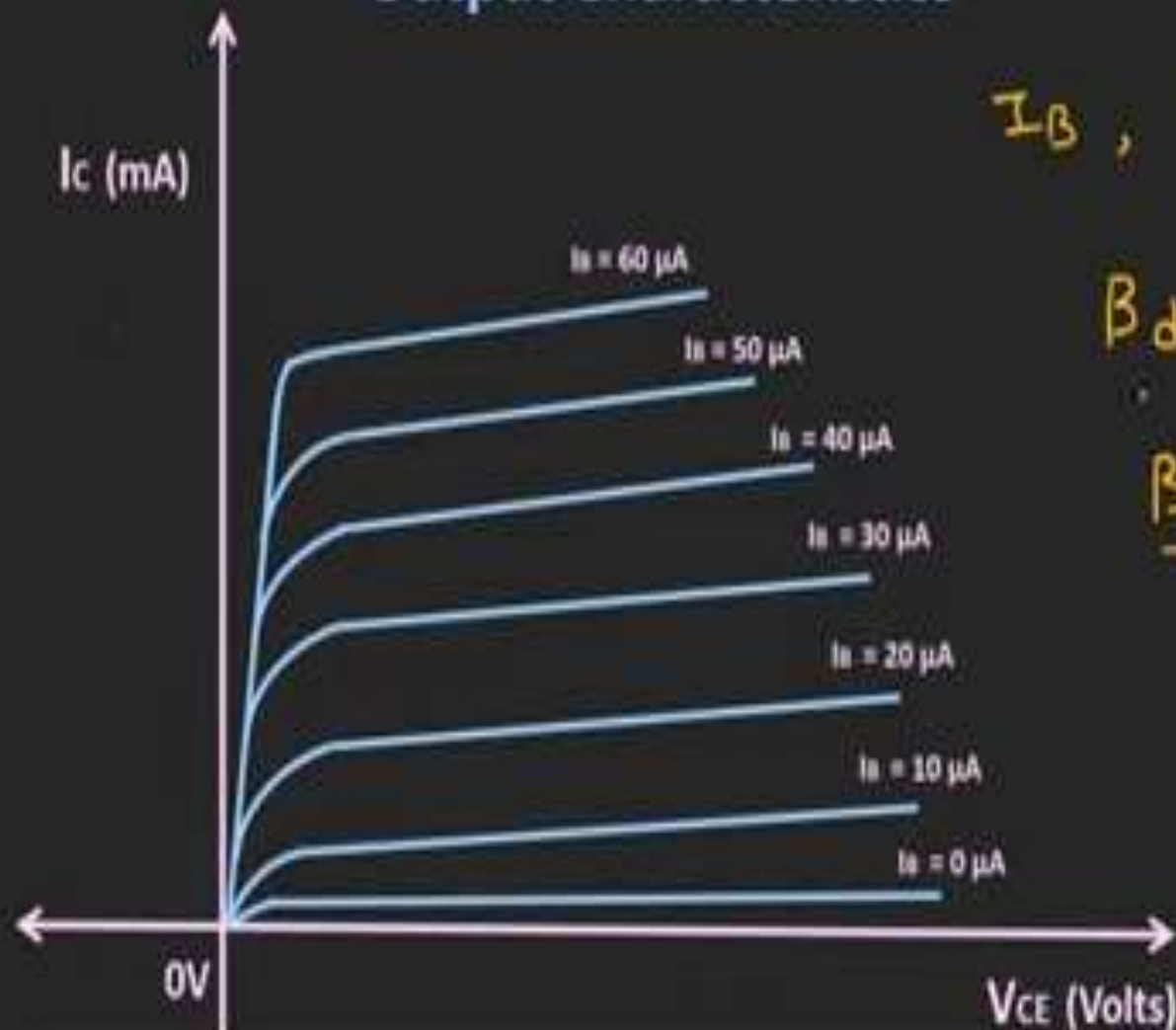


$$I_B, I_C = \beta I_B$$

$$\beta_{dc}$$

$$\beta_{dc} = \frac{\Delta I_C}{\Delta I_B}$$

Common Emitter (CE) Configuration

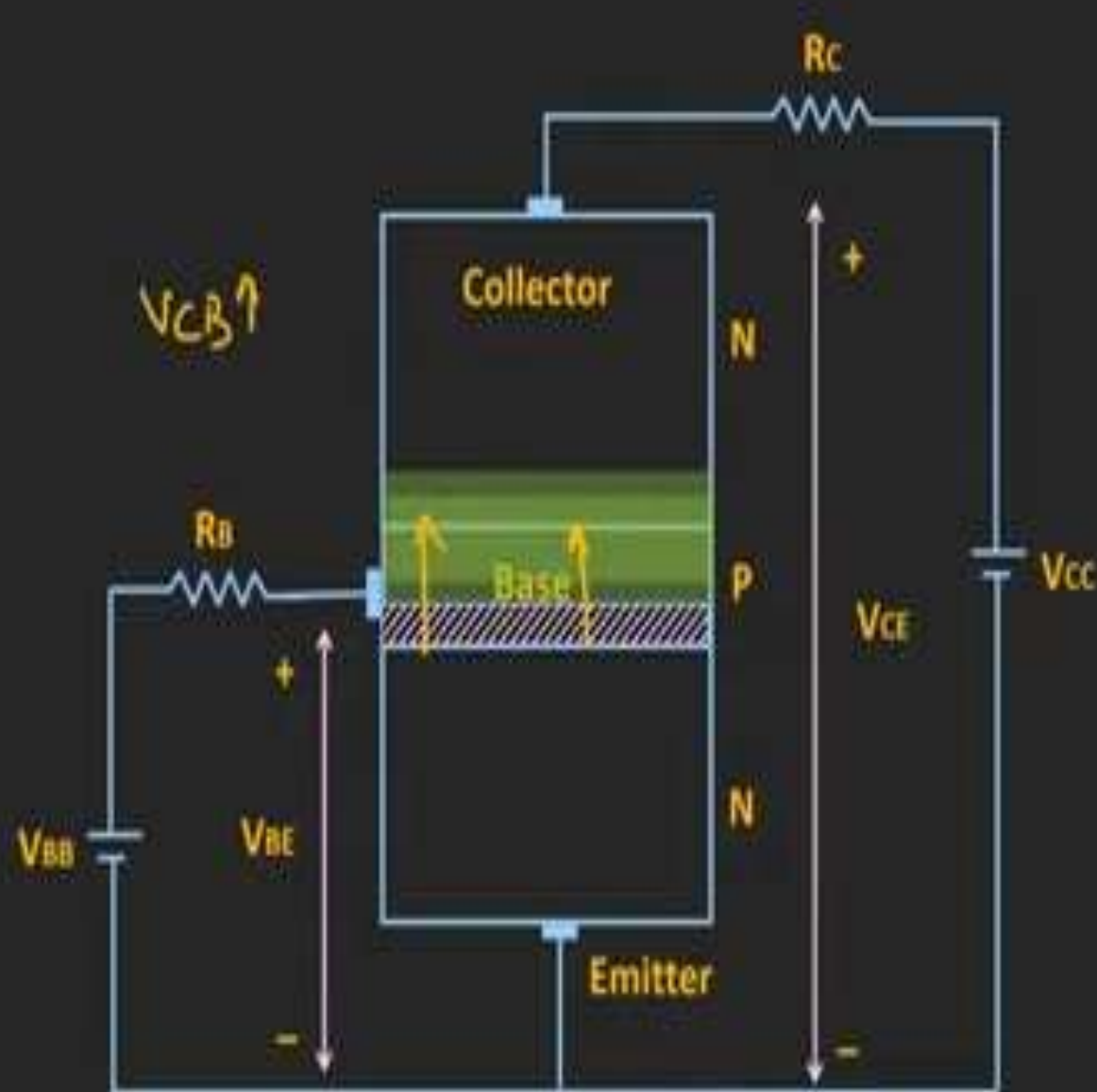


$$V_{CE} \uparrow$$

$$V_{CE} = V_{CB} + V_{BE}$$

$$V_{CE} \uparrow, I_C \uparrow$$


Common Emitter (CE) Configuration

Output Characteristics

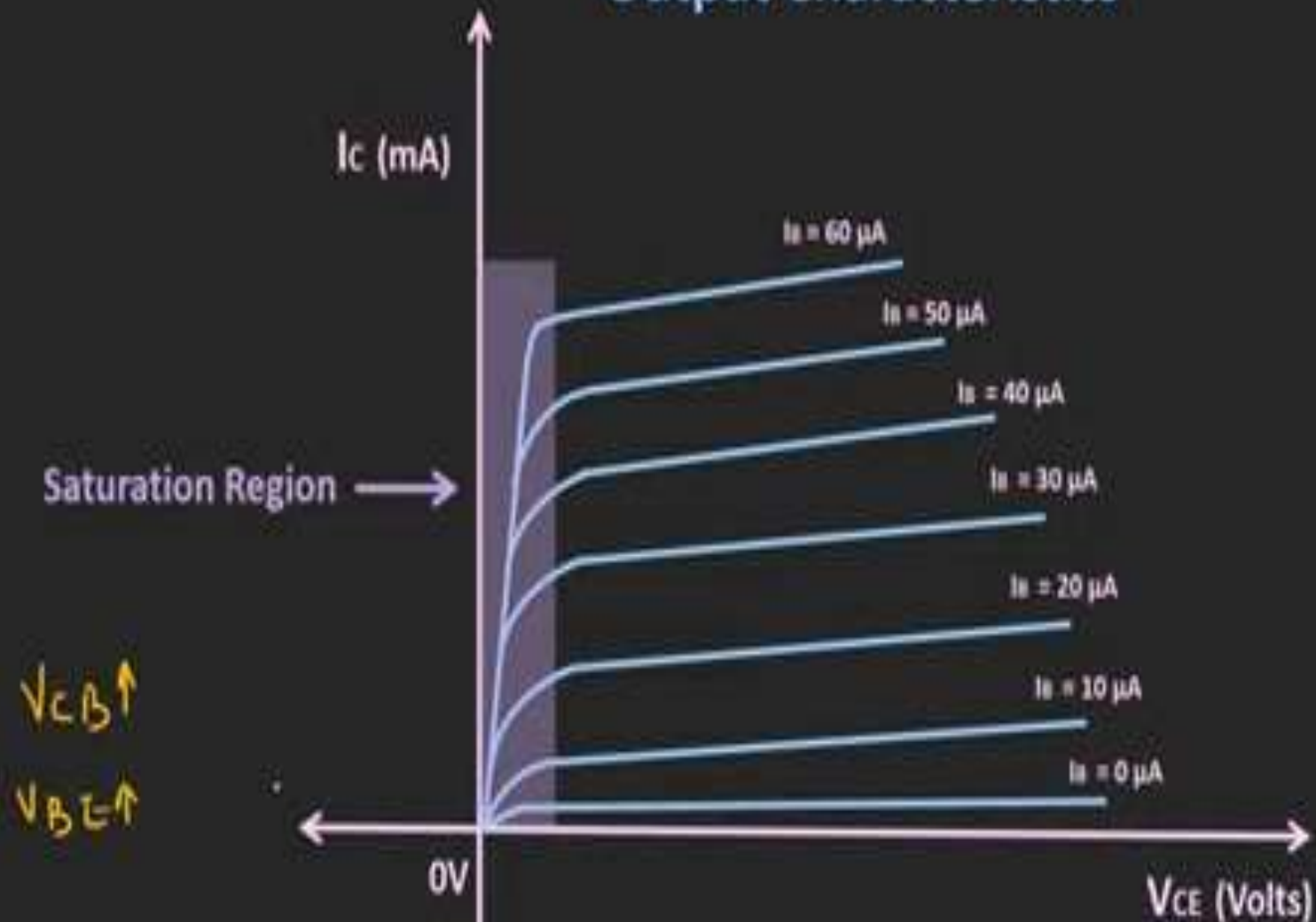

Common Emitter (CE) Configuration

Output Characteristics

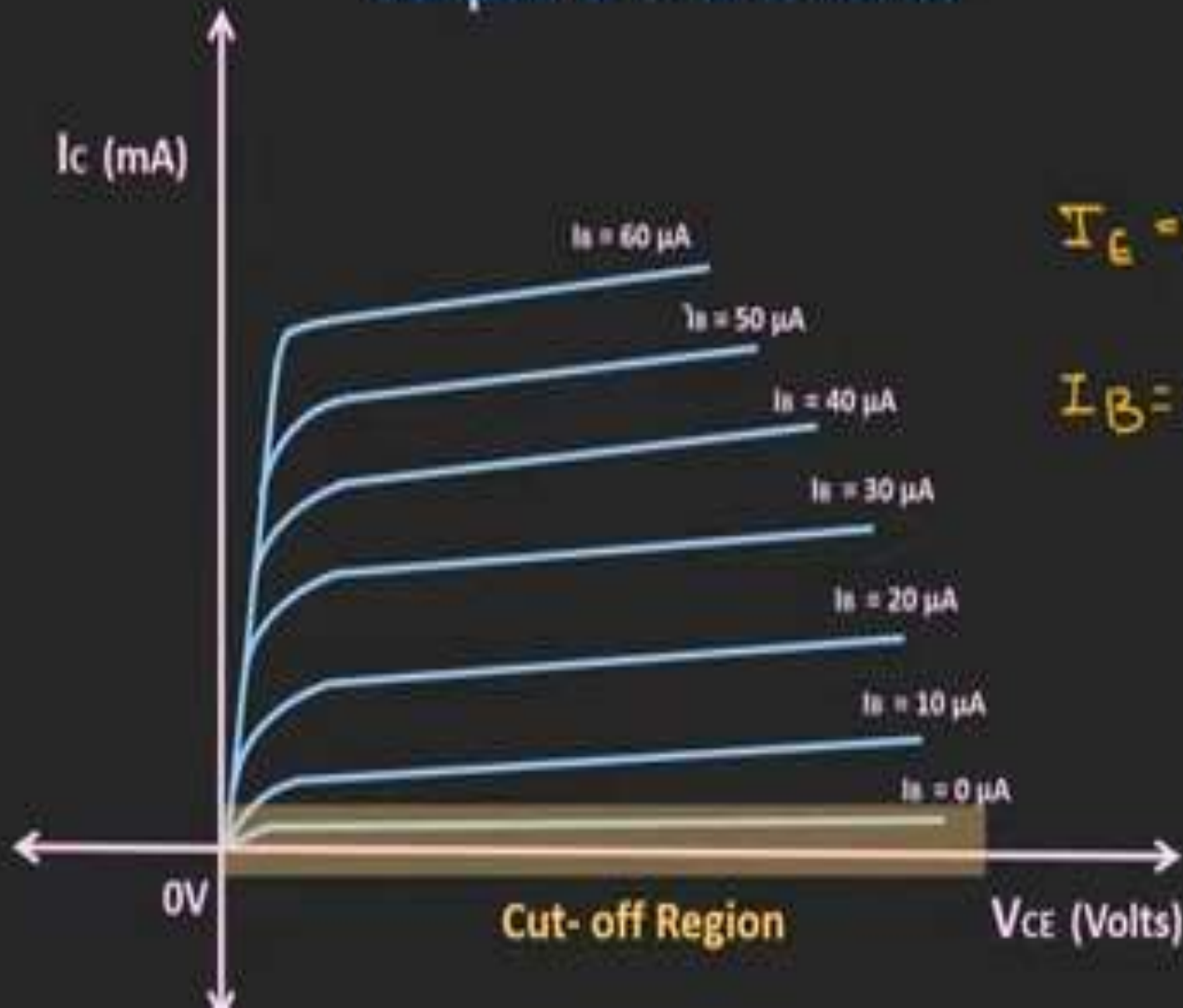


$$I_E = 0 \Rightarrow I_{CBO}$$

$$I_B = 0 \Rightarrow \underline{\hspace{2cm}}$$

Common Emitter (CE) Configuration

$$I_E = I_C + I_B$$

$$\frac{\alpha}{1-\alpha} = \beta$$

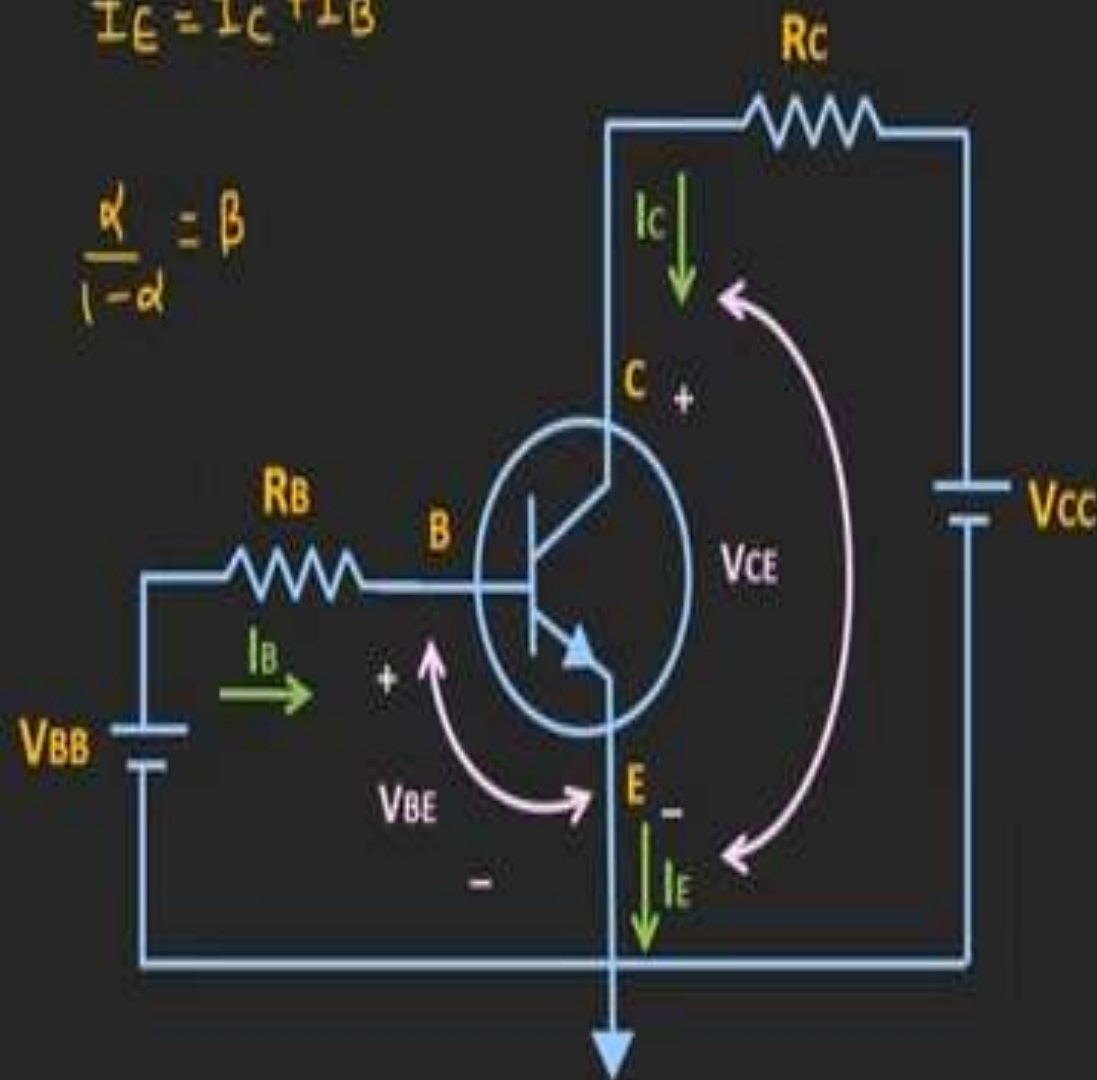

$$I_C = \alpha I_E + I_{CBO}$$

$$\Rightarrow I_C = \alpha (I_C + I_B) + I_{CBO}$$

$$\Rightarrow (1-\alpha)I_C = \alpha I_B + I_{CBO}$$

$$\Rightarrow I_C = \frac{\alpha}{1-\alpha} I_B + \frac{1}{1-\alpha} I_{CBO}$$

$$\Rightarrow I_C = \beta I_B + \frac{1}{1-\alpha} I_{CBO}$$




Common Emitter (CE) Configuration

$$0.95 \rightarrow 0.99$$


$$\beta = \frac{\alpha}{1-\alpha} \Rightarrow \beta + 1 = \frac{1}{1-\alpha}$$

$$= \frac{1}{1-\alpha} I_{CQ}$$

$$= (\beta + 1) I_{CQ}$$

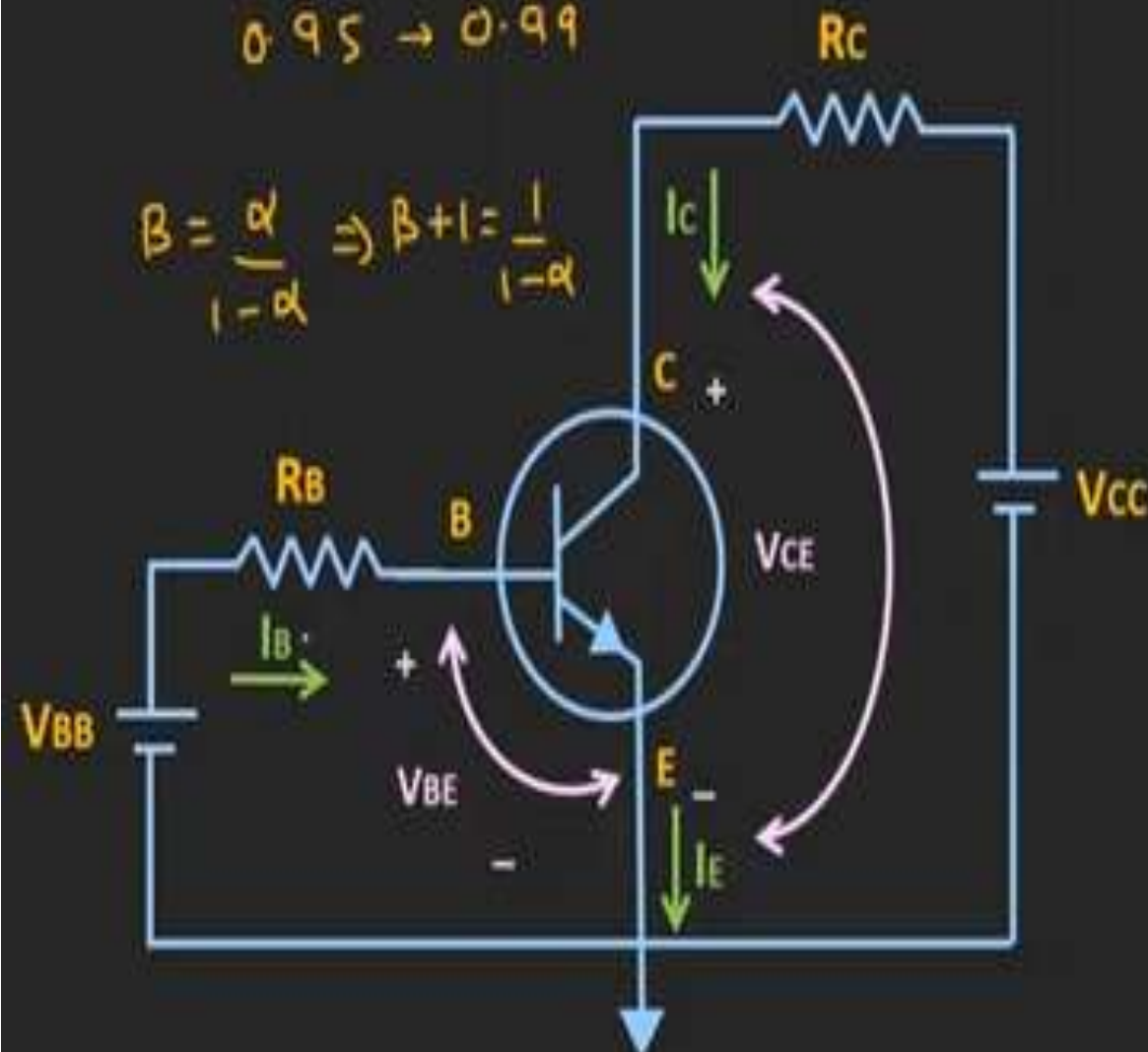

Common Emitter (CE) Configuration

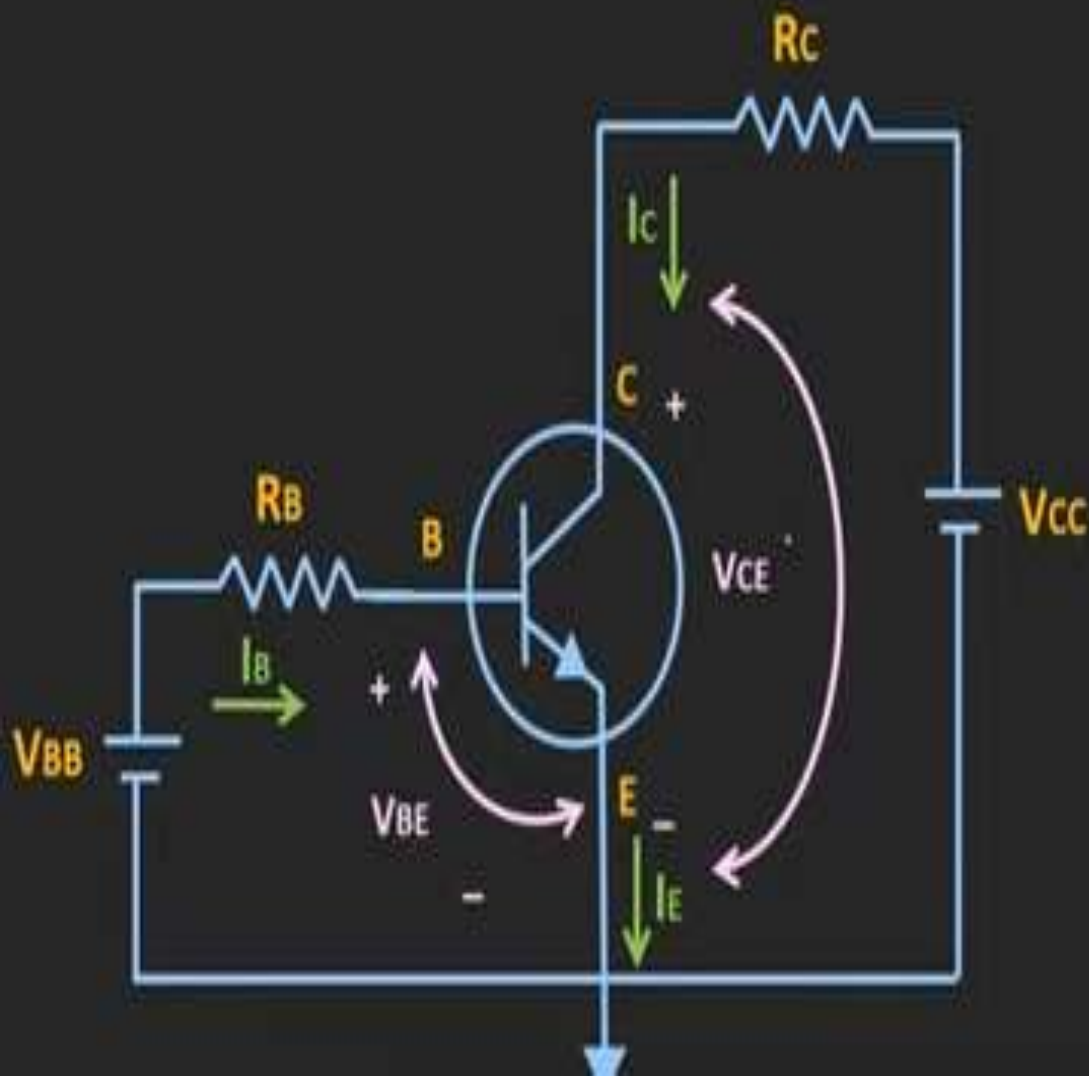

Moderate Current Gain


Moderate Voltage Gain

High Power Gain

Moderate Input Impedance

Moderate Output Impedance

Common Emitter (CE) Configuration

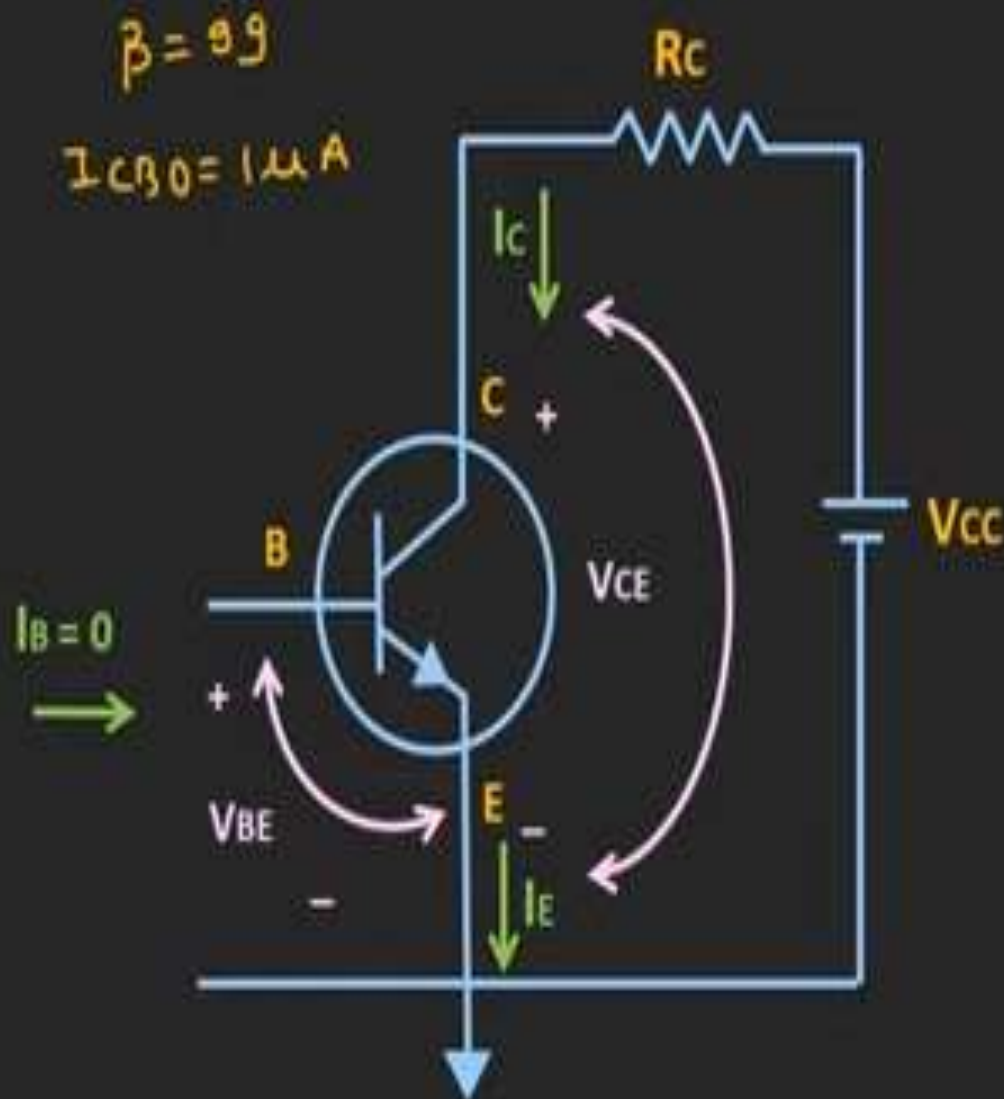


$$I_{CE0} = (\beta + 1) I_{CB0}$$

$$I_{CE0} = 100 \mu A$$


BJT

Common Collector Configuration

Common Collector (CC) Configuration

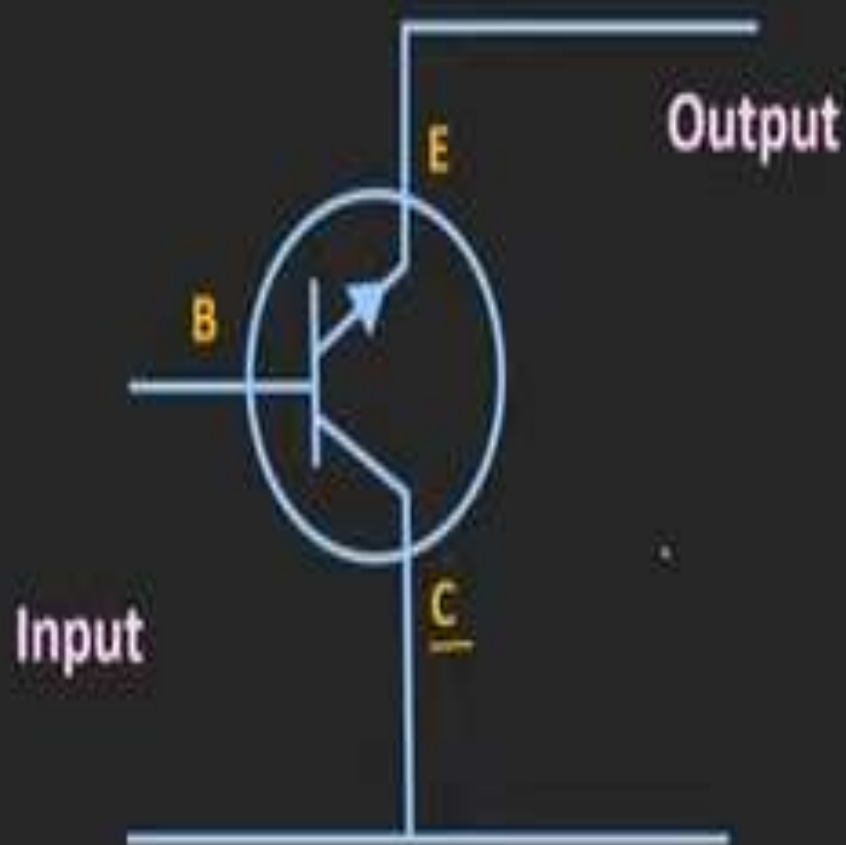


Common Collector (CC) Configuration

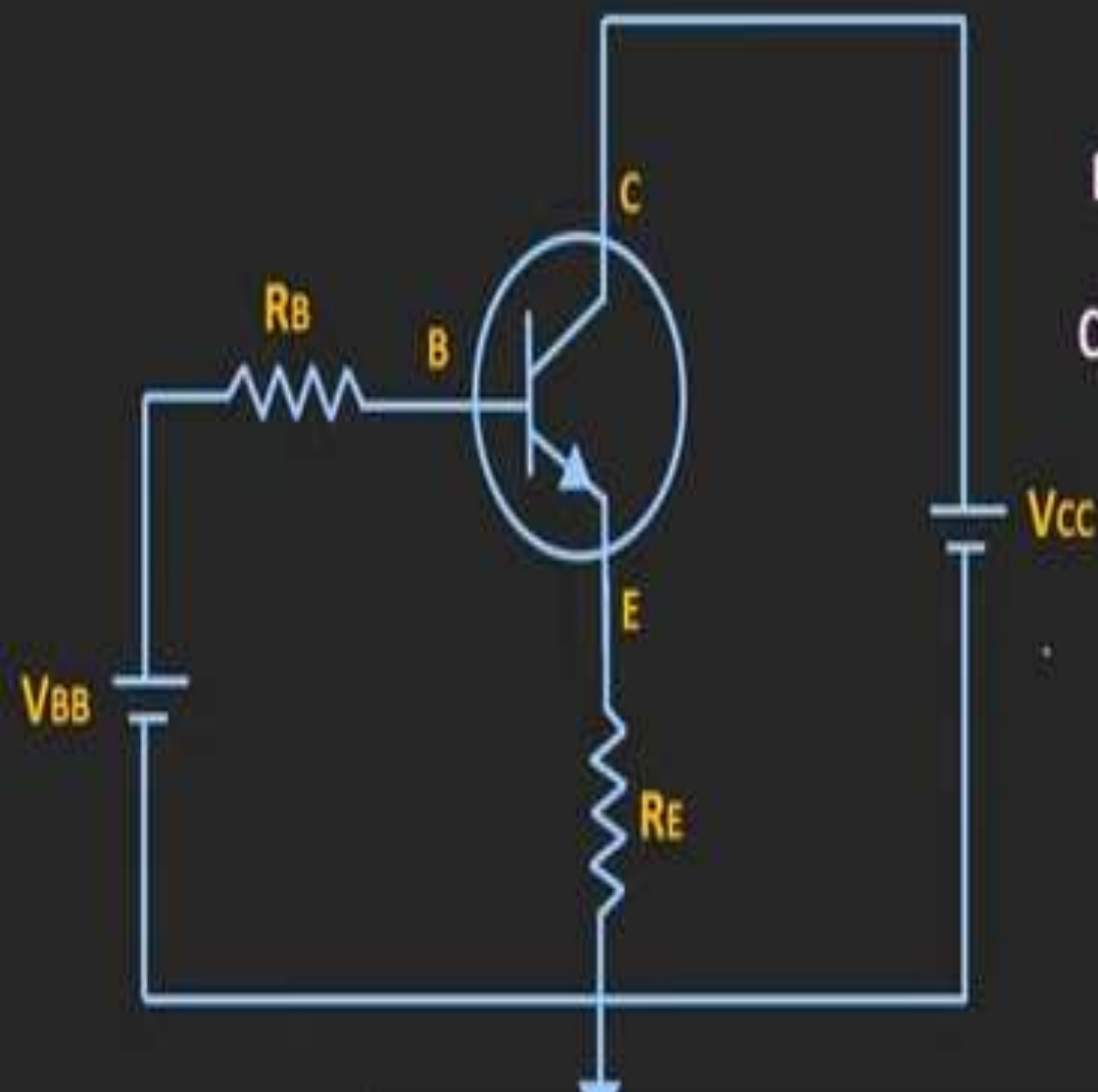


Base- Emitter Junction - Forward Bias

Collector- Base Junction - Reverse Bias

Common Collector (CC) Configuration

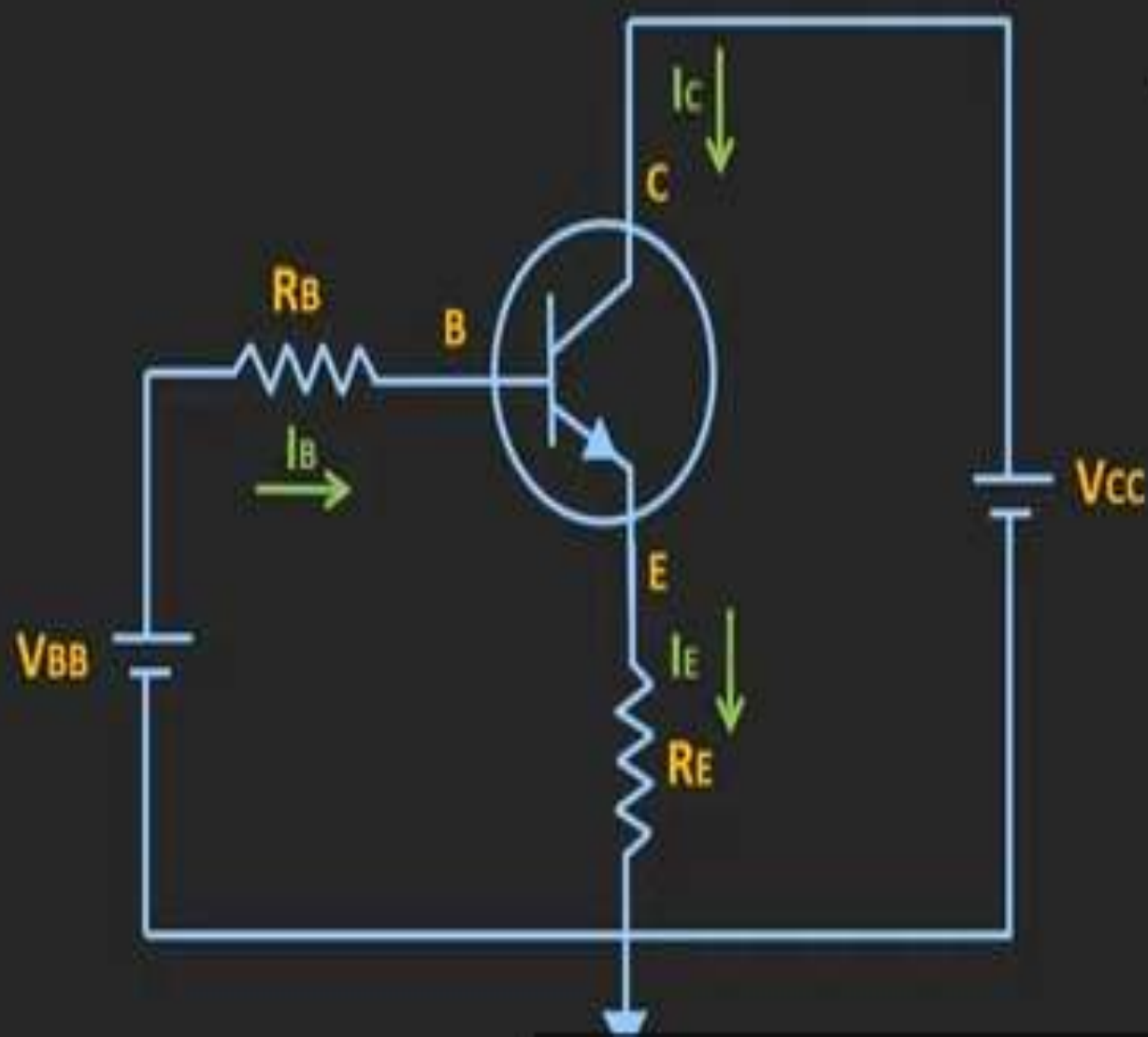

Common Collector (CC) Configuration

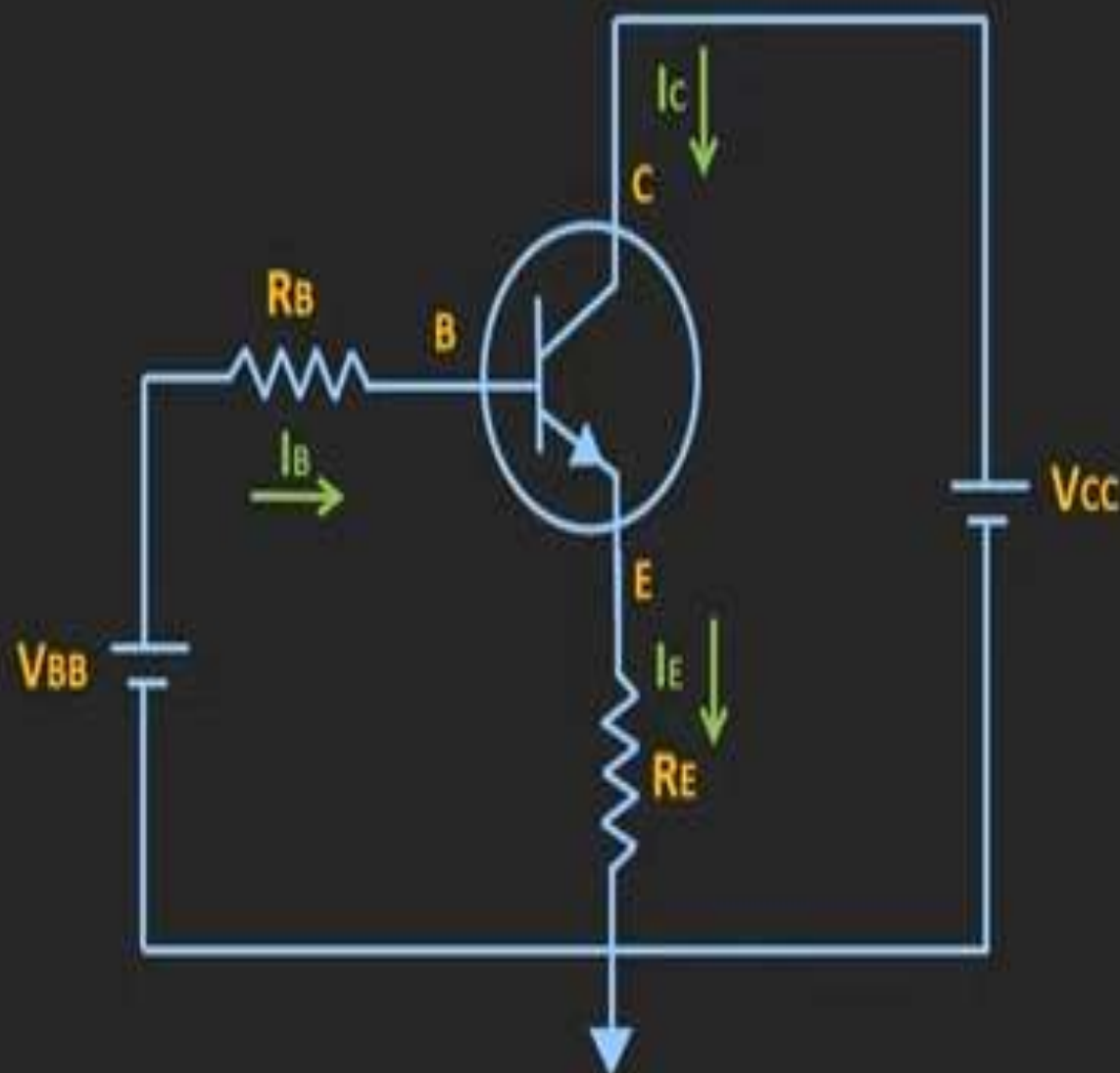

Input Characteristics

V_{CB}, I_B

Output Characteristics


V_{CE}, I_E

Common Collector (CC) Configuration

Output Characteristics


$$I_E = \alpha I_C$$

$$I_E \approx I_C$$

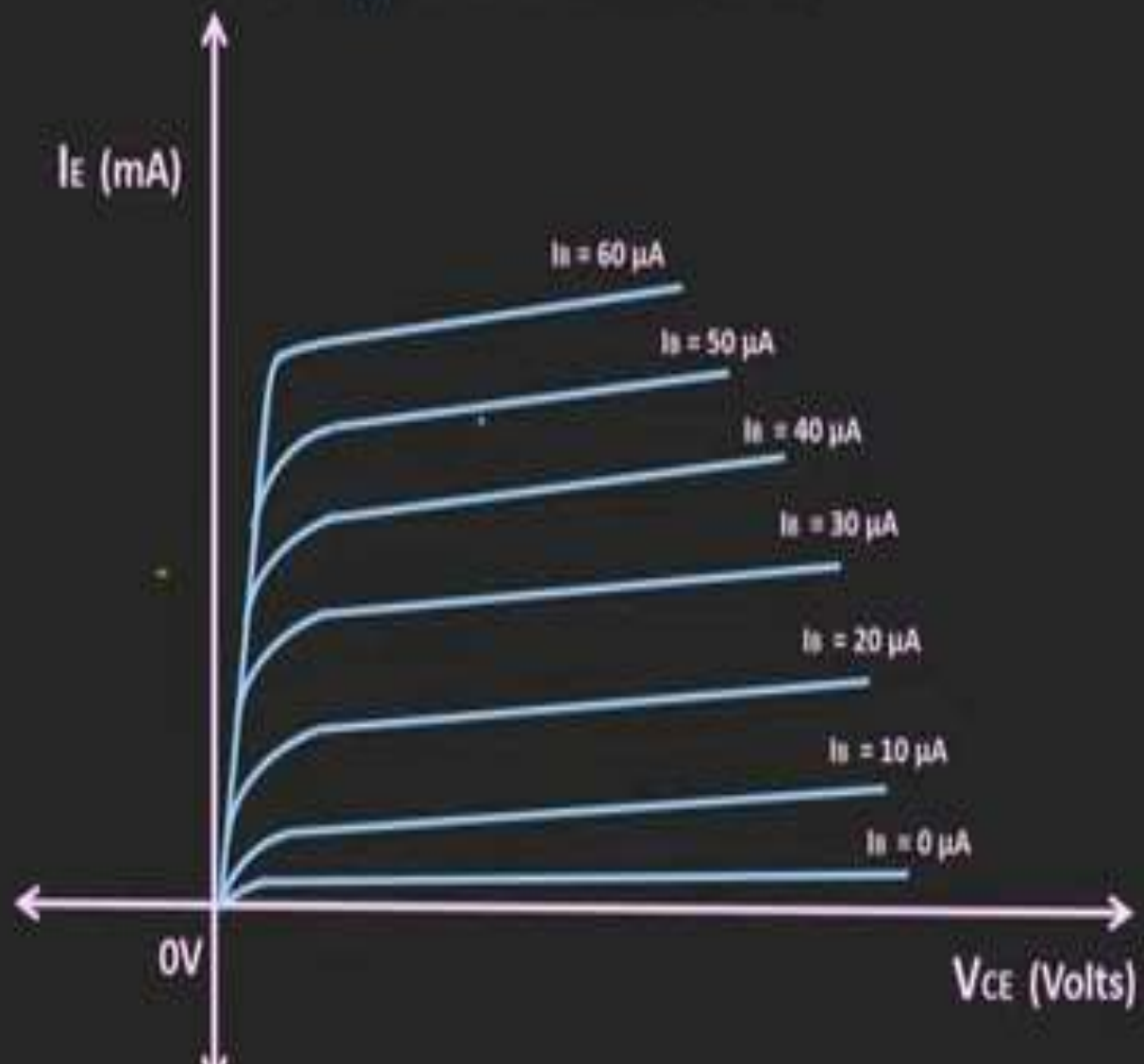

Common Collector (CC) Configuration


Input Characteristics

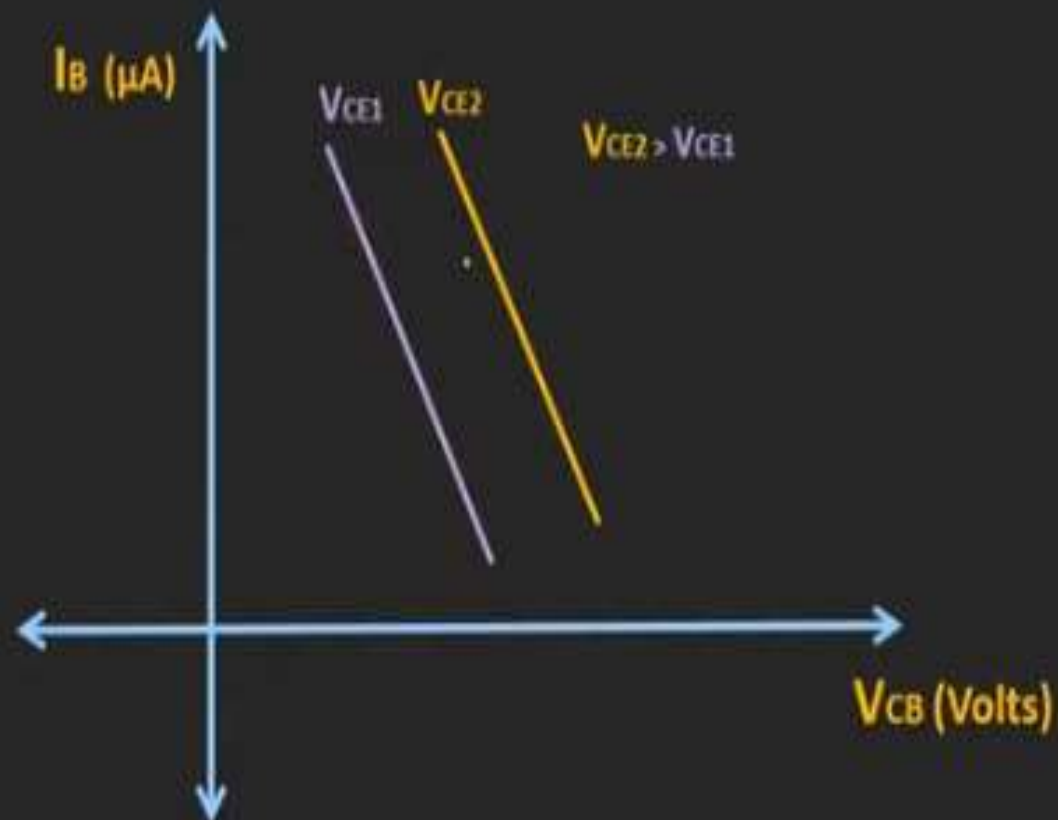


Common Collector (CC) Configuration

$$V_{CE} = V_{CB} + V_{BE}$$

$$I_B \downarrow$$

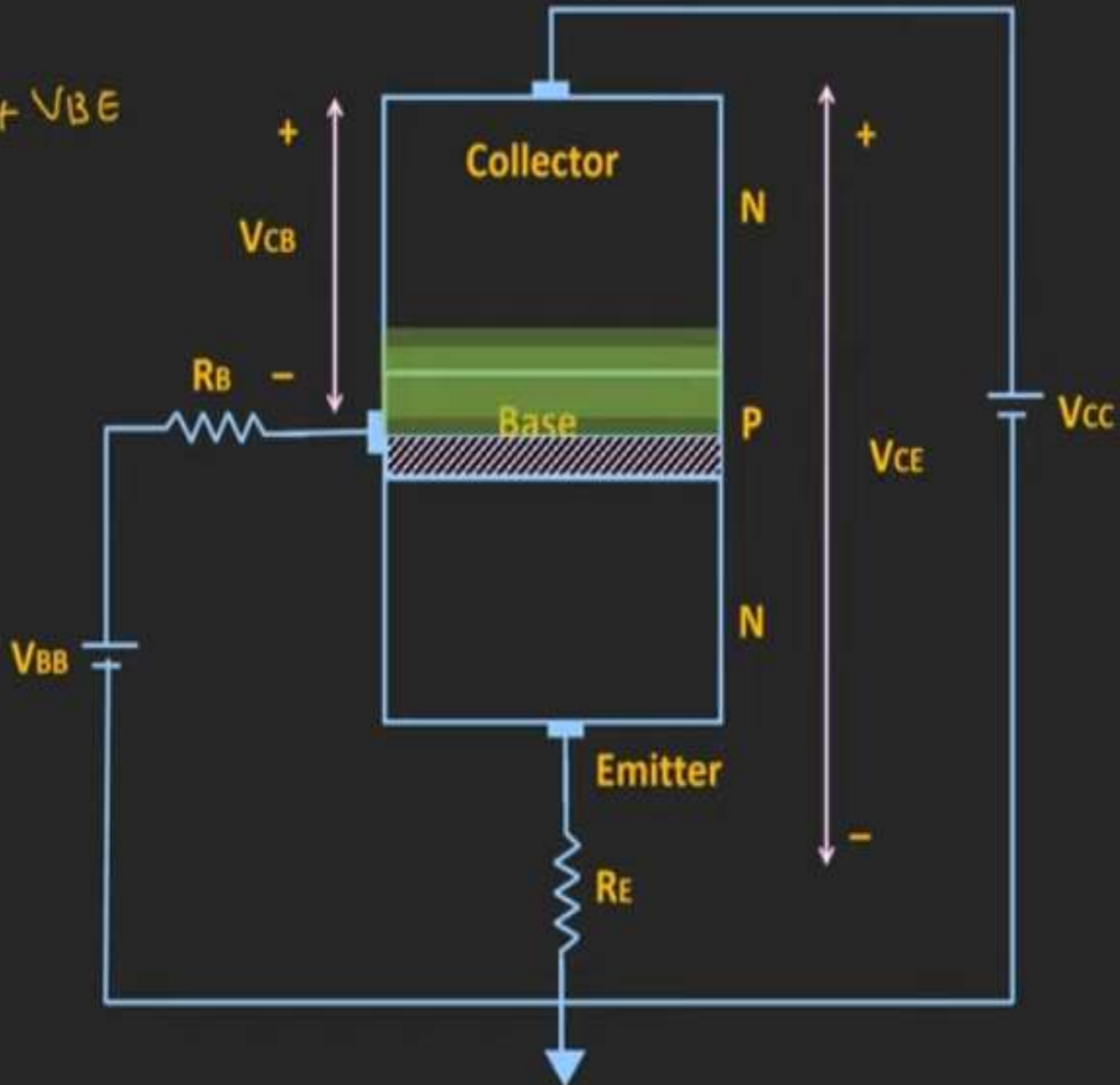

Common Collector (CC) Configuration

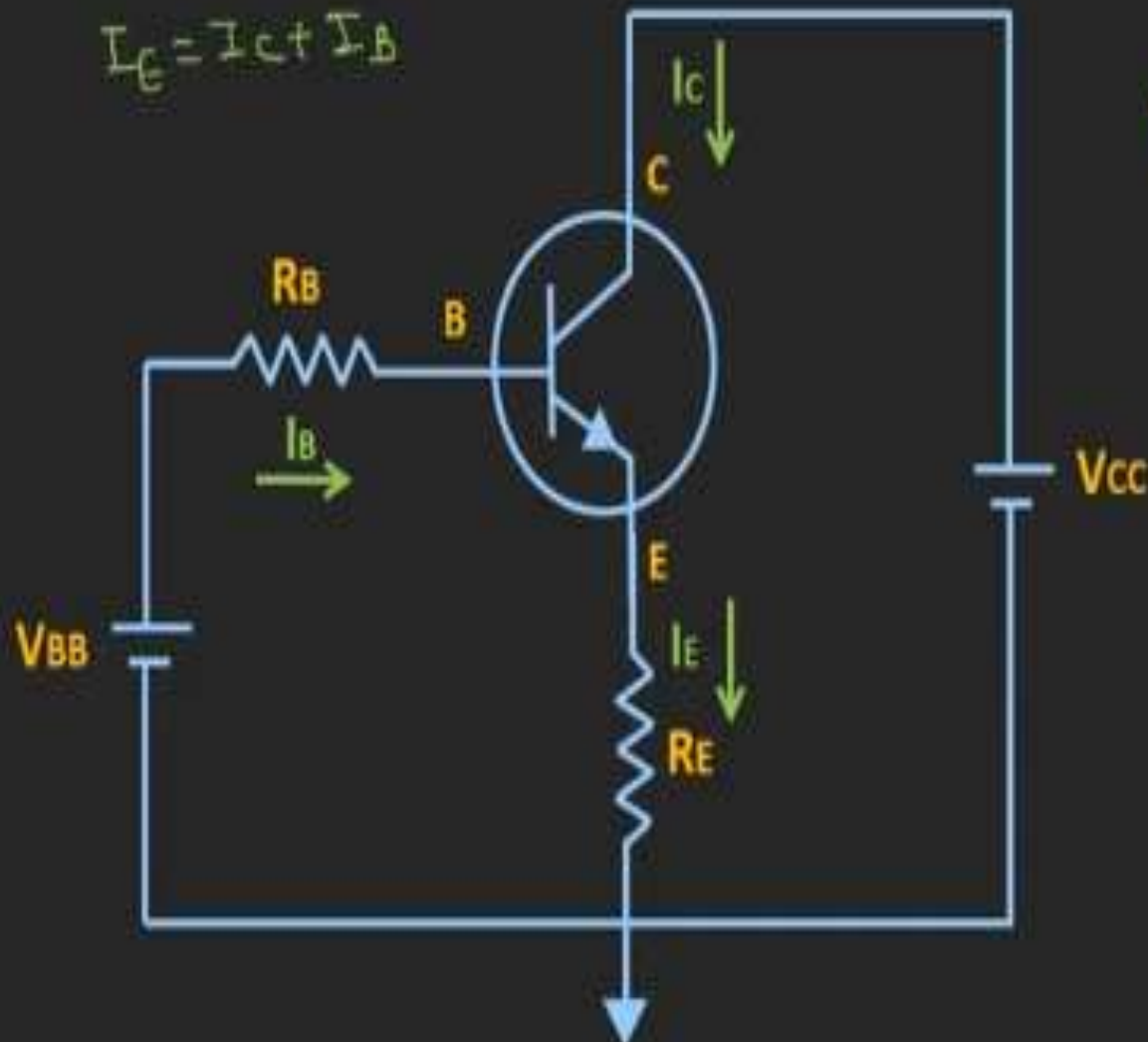

$$I_E = I_C + I_B$$

$$\gamma = \frac{I_E}{I_B}$$


$$I_C \approx \beta I_B$$

$$\alpha, \beta, \gamma$$

$$\gamma = \frac{I_C + I_B}{I_B}$$

$$\gamma = \frac{I_C}{I_B} + 1 \approx \beta + 1$$

Common Collector (CC) Configuration

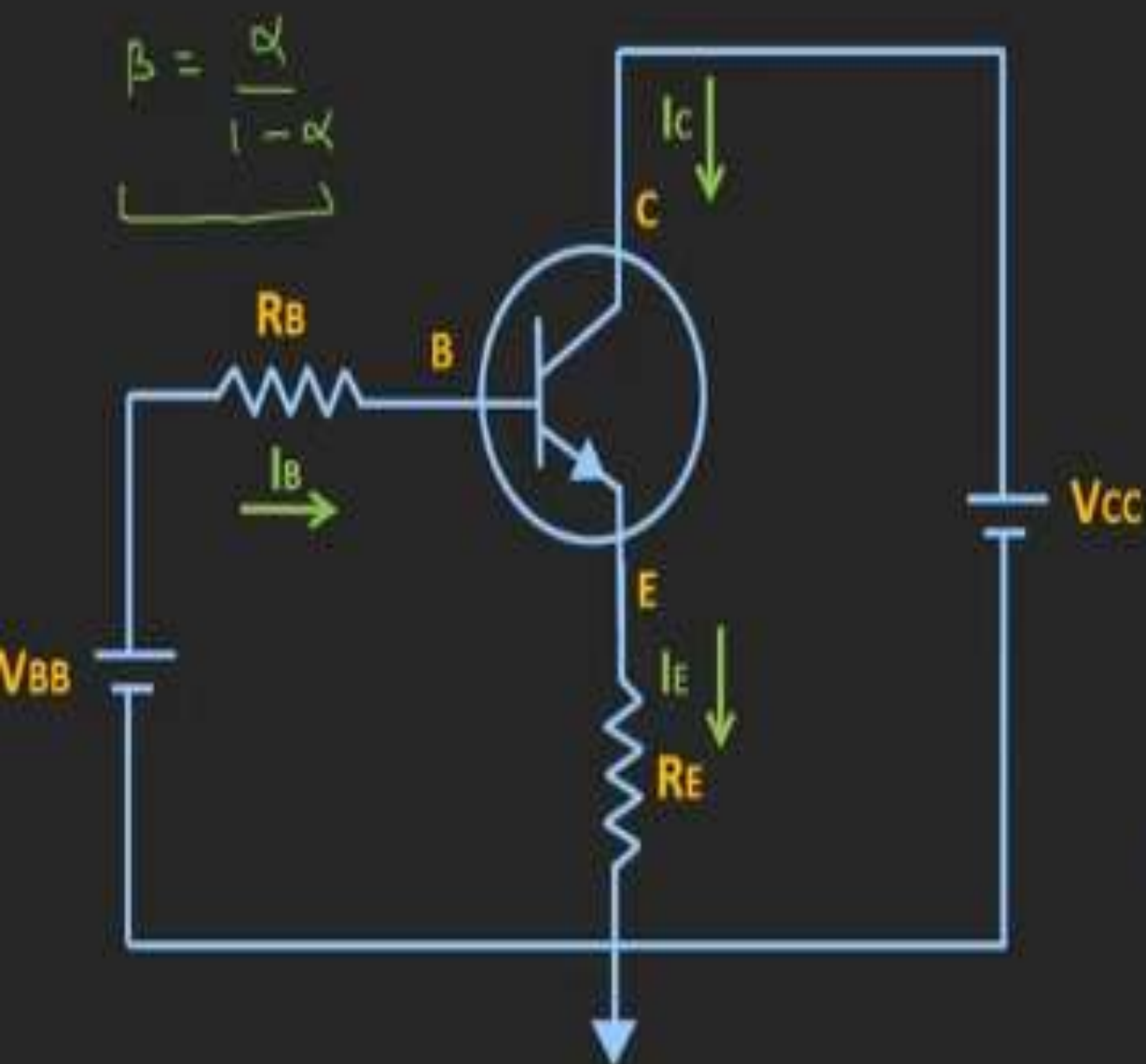


$$\therefore \gamma = \beta + 1$$

$$= \frac{\alpha}{1 - \alpha} + 1 = \frac{1}{1 - \alpha}$$

$$\therefore \gamma = \beta + 1 = \frac{1}{1 - \alpha}$$

$$\alpha \cdot \gamma = \frac{1 \cdot \alpha}{1 - \alpha} \Rightarrow \alpha \cdot \gamma = \beta$$

Common Collector (CC) Configuration

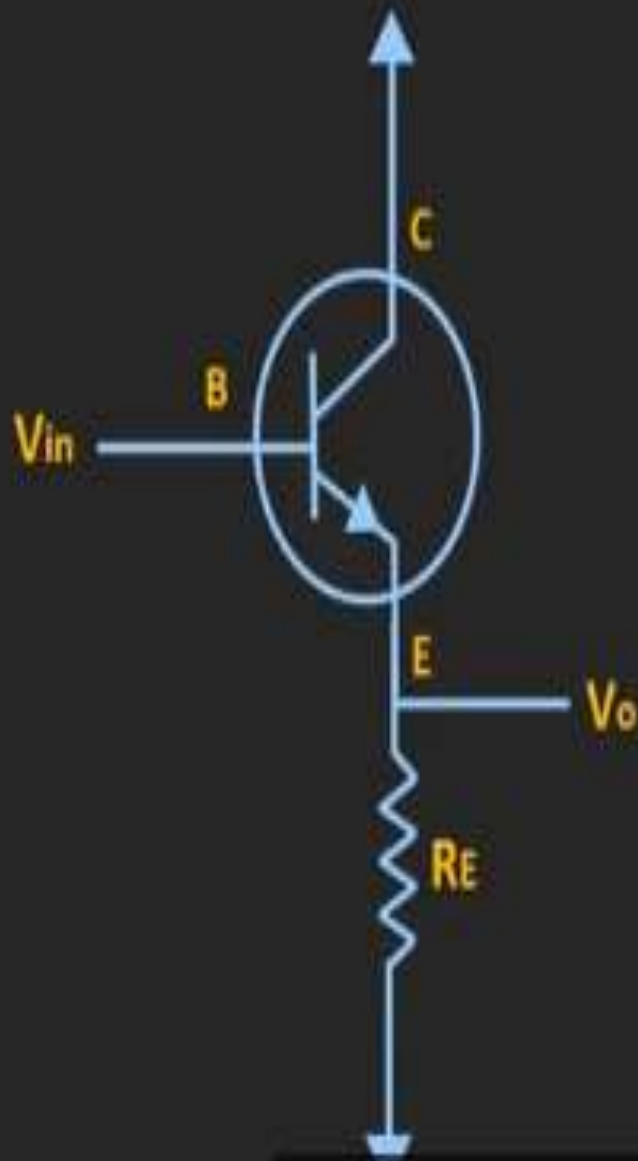

High Input Impedance

Low Output Impedance

$$\beta + 1$$

High Current Gain

$$\approx 1$$


Low Voltage Gain

Low Power Gain

BJT


Common Base Configuration

Common Base (CB) Configuration

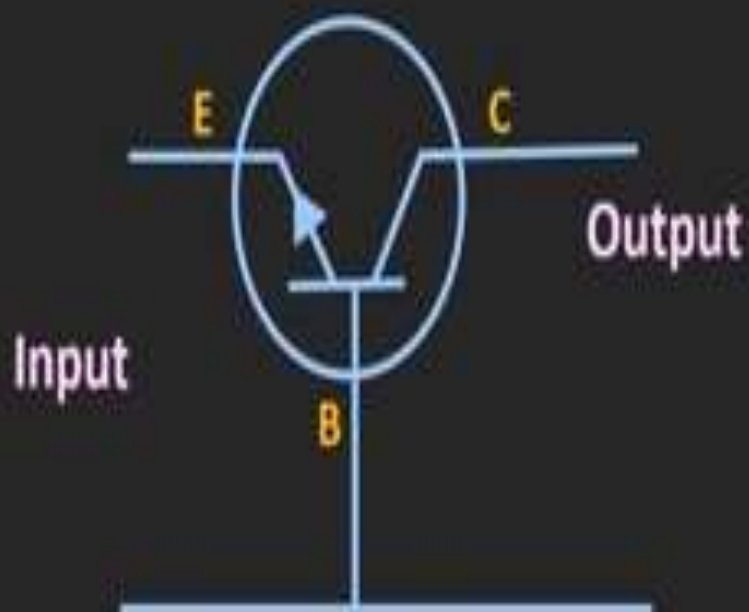

Common Base (CB) Configuration

NPN Transistor

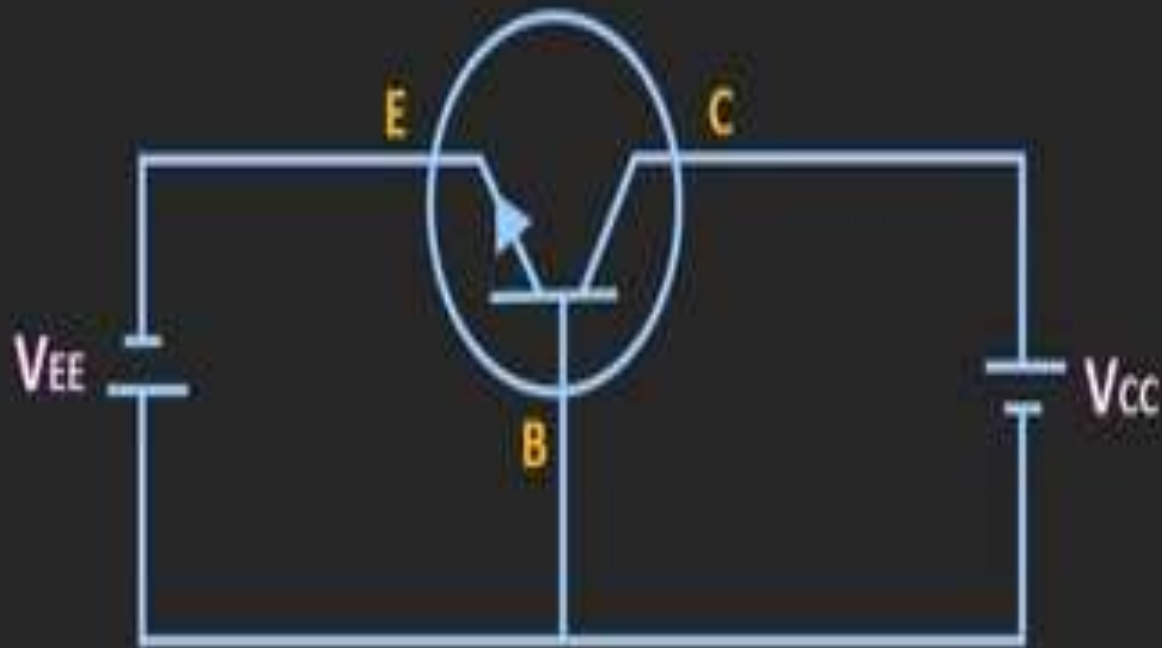


Forward Bias

Reverse Bias

Common Base (CB) Configuration

NPN Transistor

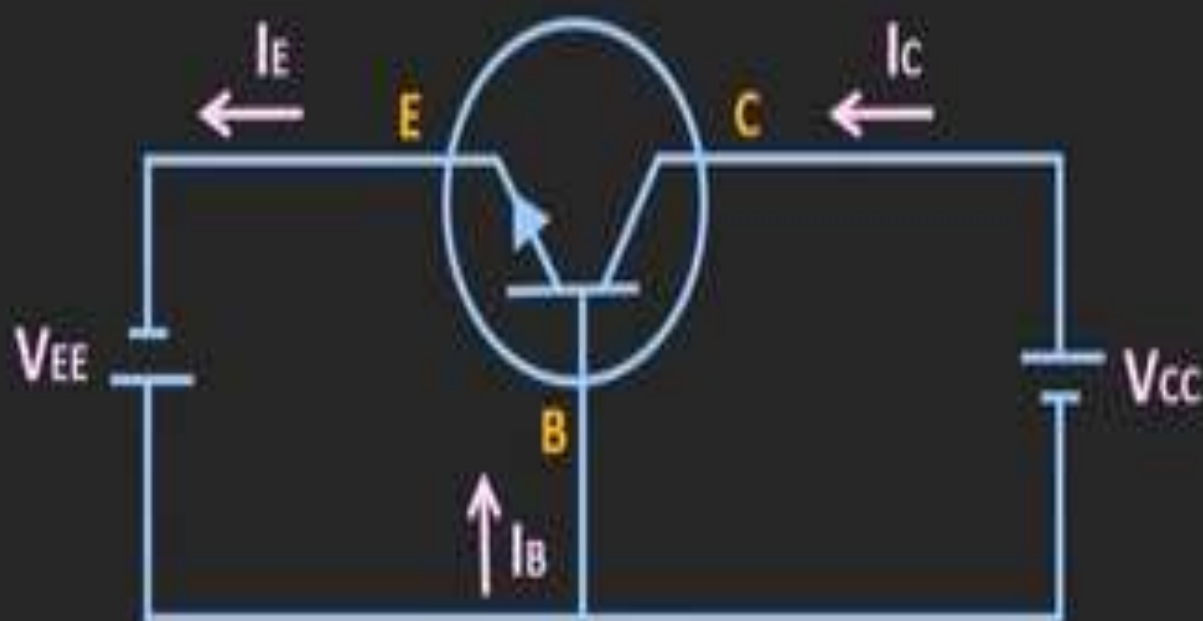


Forward Bias

Reverse Bias

Common Base (CB) Configuration

PNP Transistor

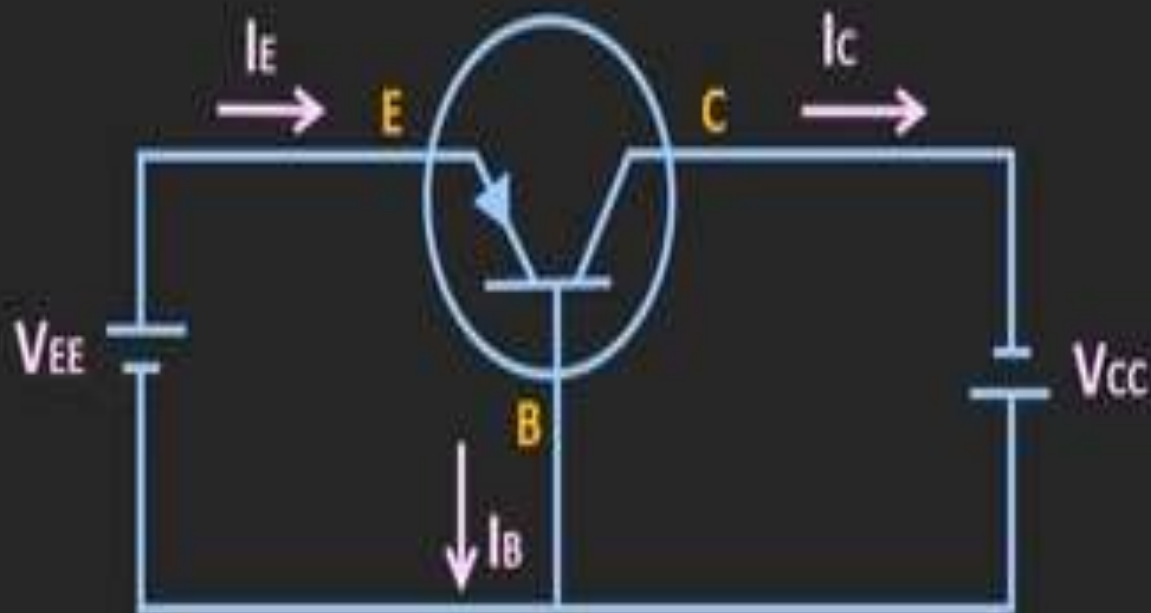


Forward Bias

Reverse Bias

Common Base (CB) Configuration

PNP Transistor

$$I_E = I_B + I_C$$

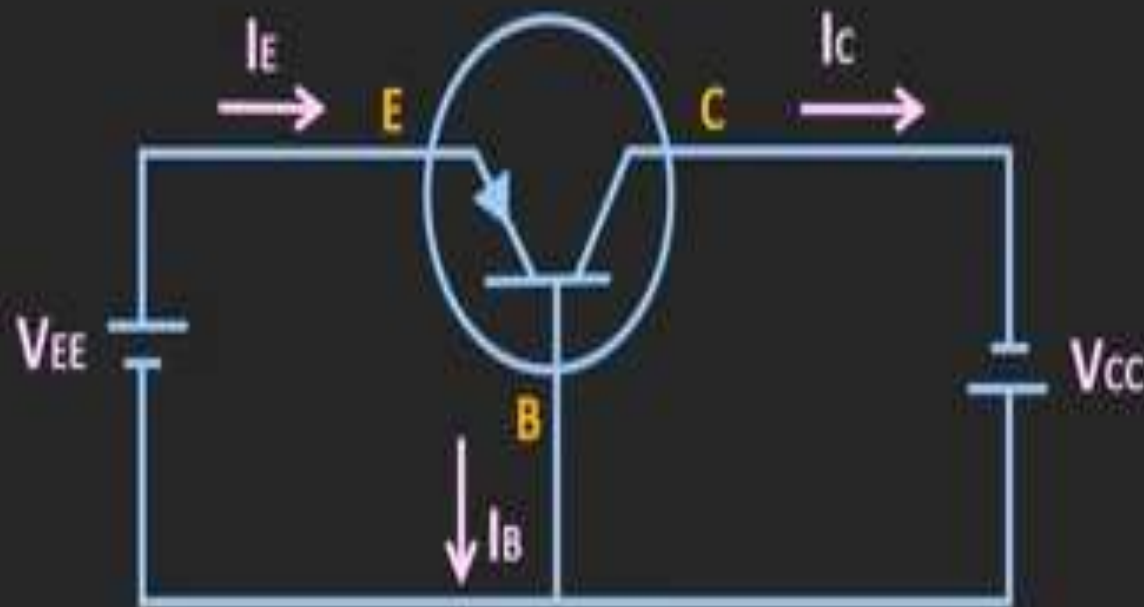

Forward Bias

Reverse Bias


Common Base (CB) Configuration

NPN Transistor

Input Characteristics

I_E, V_{BE}

Output Characteristics

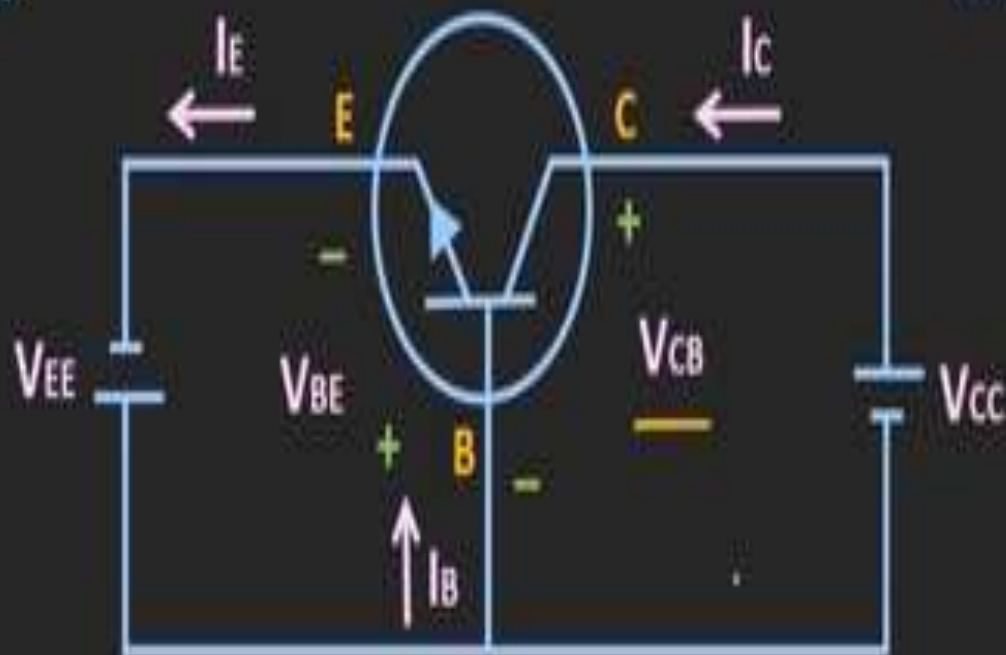


Forward Bias

Reverse Bias


Common Base (CB) Configuration

Input Characteristics

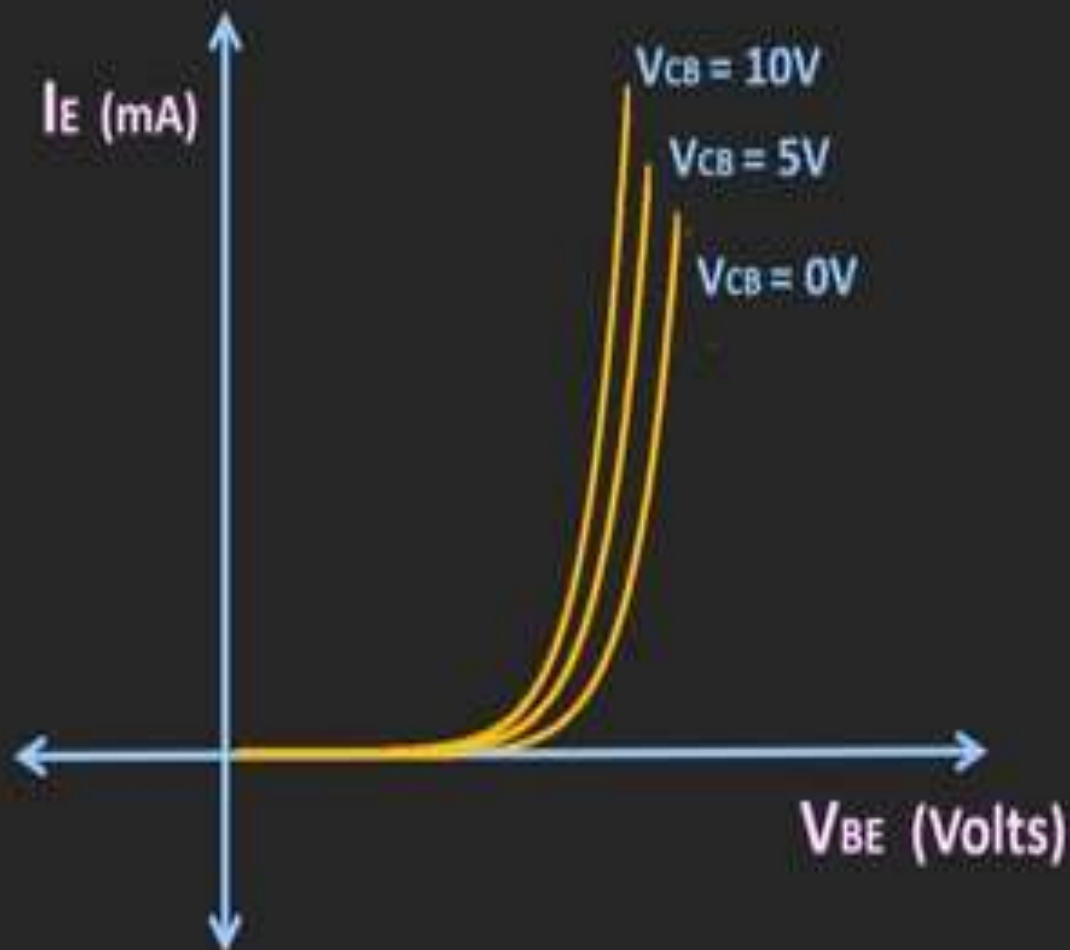

Common Base (CB) Configuration

Input Characteristics

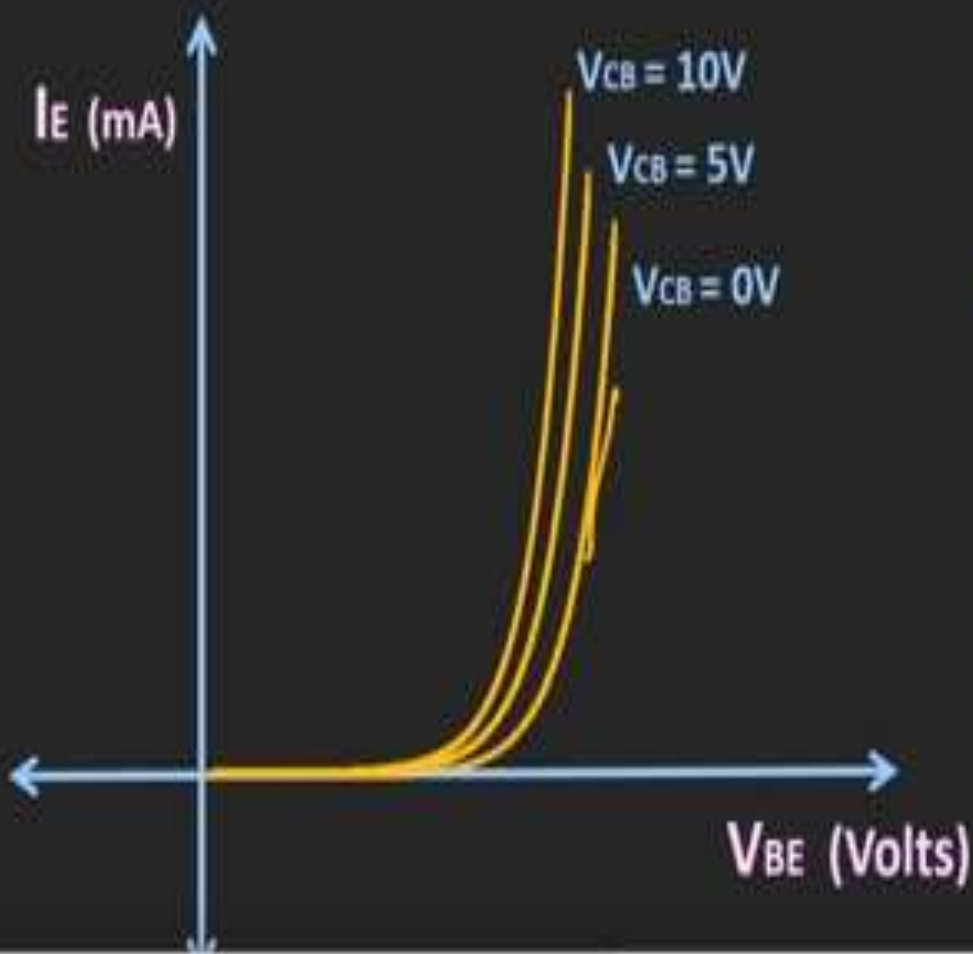

$$R_{in} = \frac{\Delta V_{BE}}{\Delta I_E}$$




Common Base (CB) Configuration

NPN Transistor

Input Characteristics

Output Characteristics

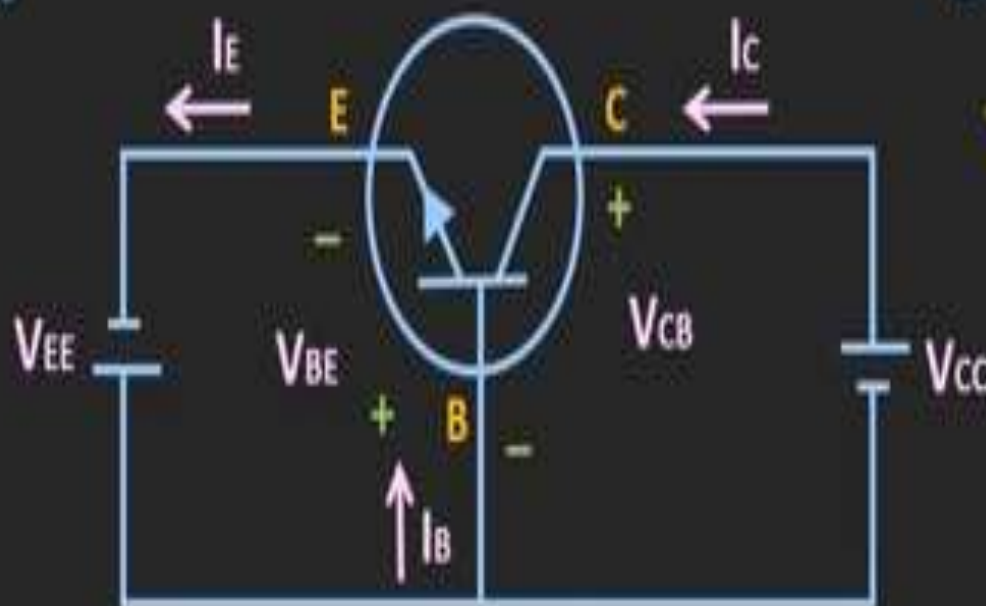


I_C, V_{CB}

Forward Bias

Reverse Bias


Common Base (CB) Configuration

Output Characteristics

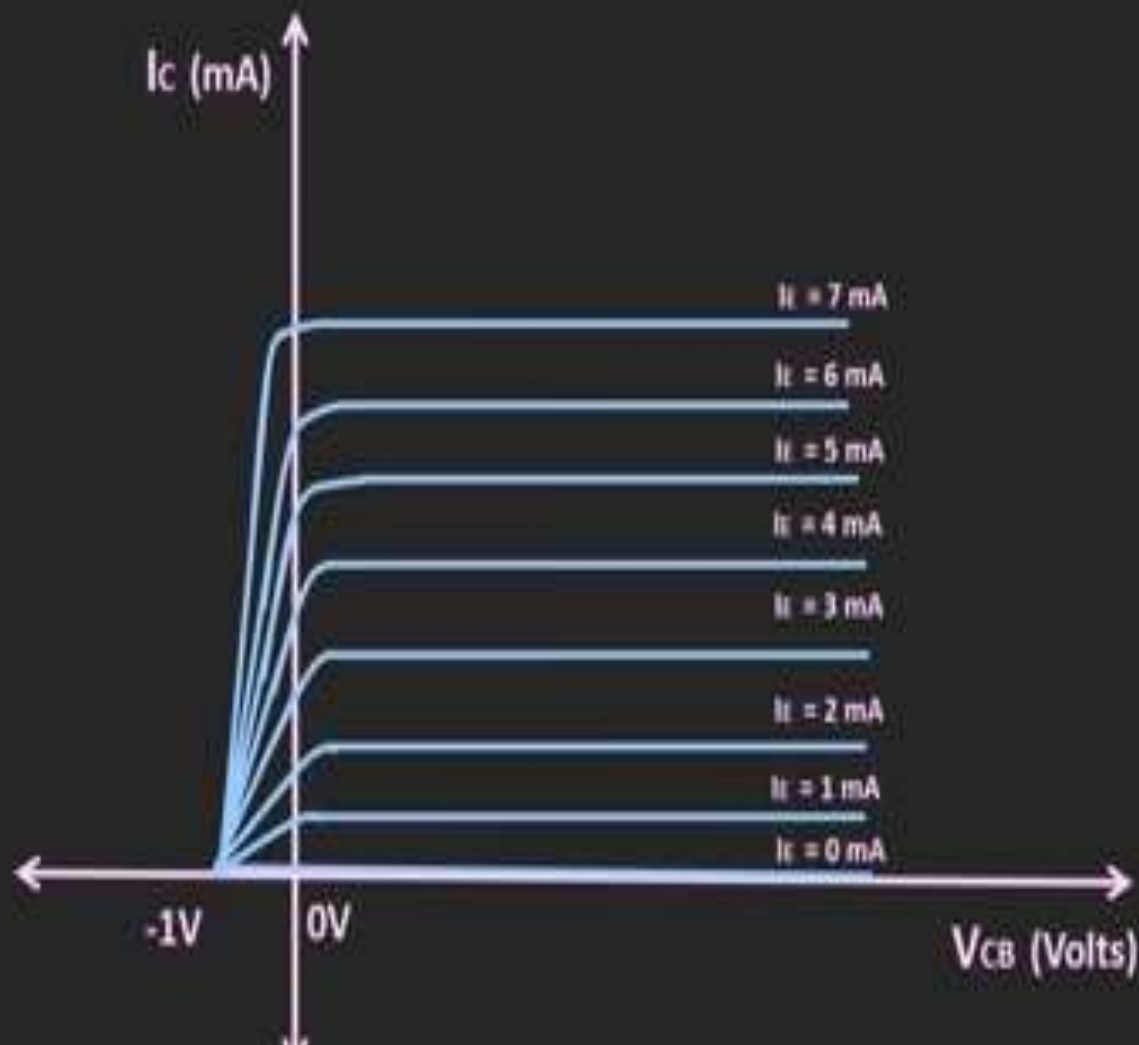


Common Base (CB) Configuration


Output Characteristics

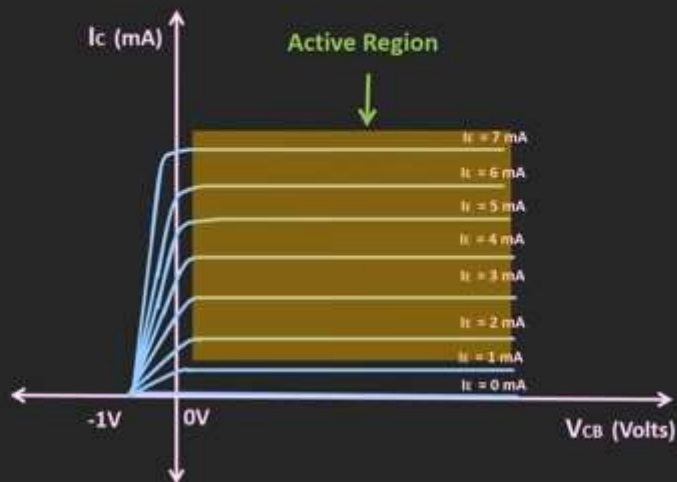

Output Characteristics

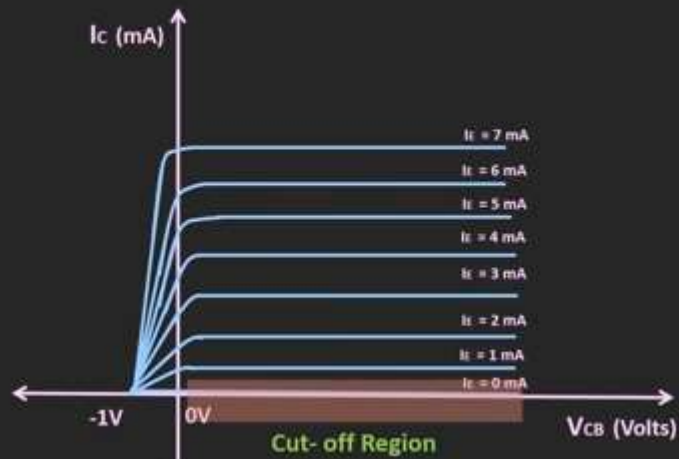


Output Characteristics

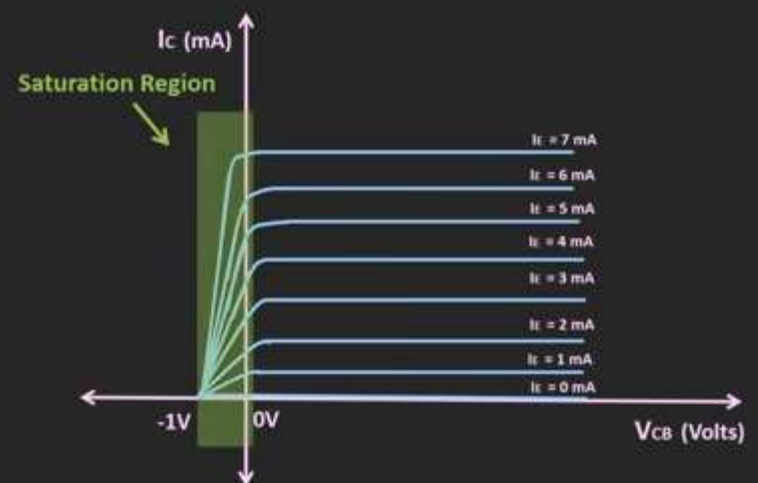

Common Base (CB) Configuration

Output Characteristics

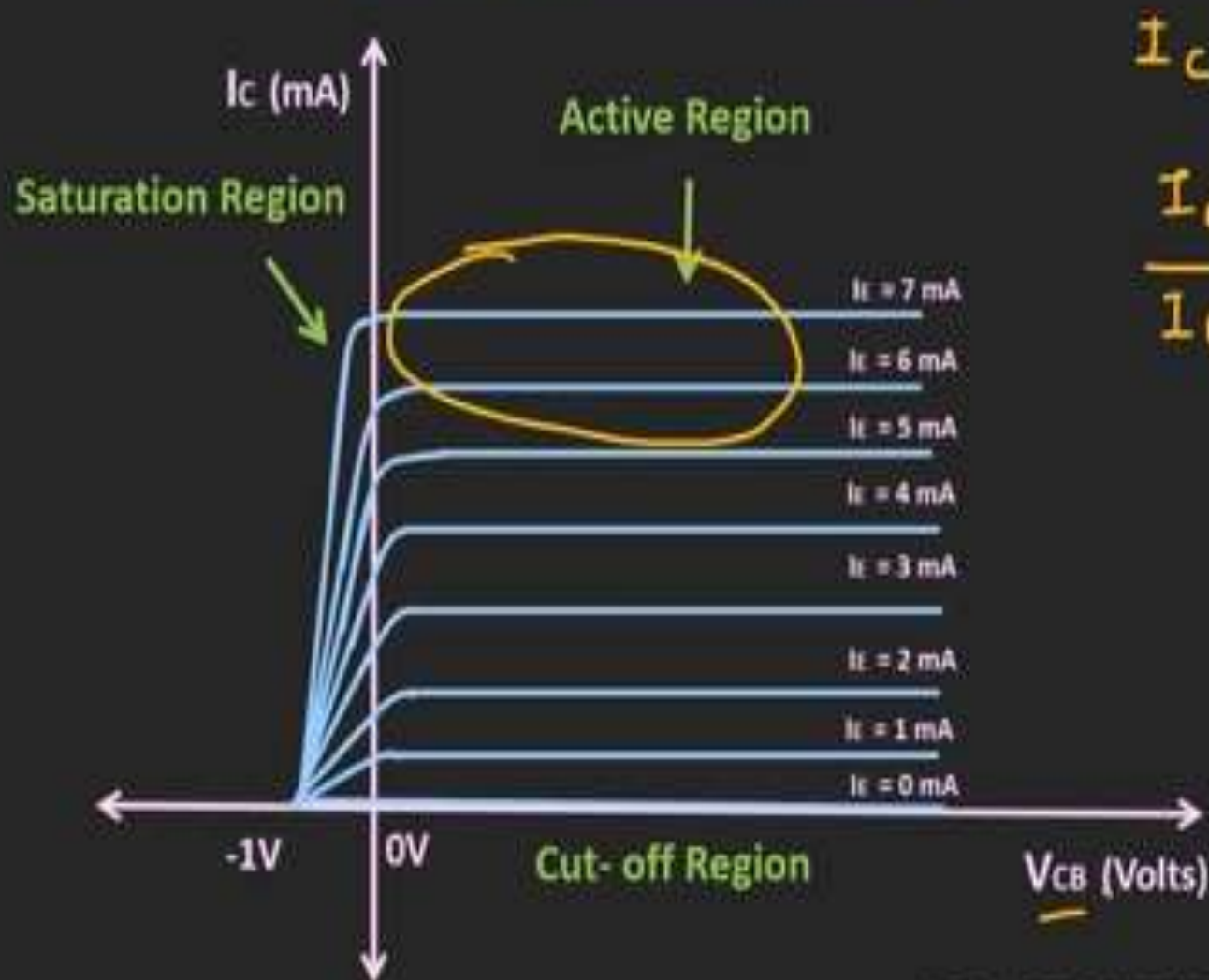


$$I_c = \alpha I_e$$

$$\frac{I_c}{I_e} = \alpha$$


Common Base (CB) Configuration

NPN Transistor

$$I_{CT} = I_C + I_{CO}$$

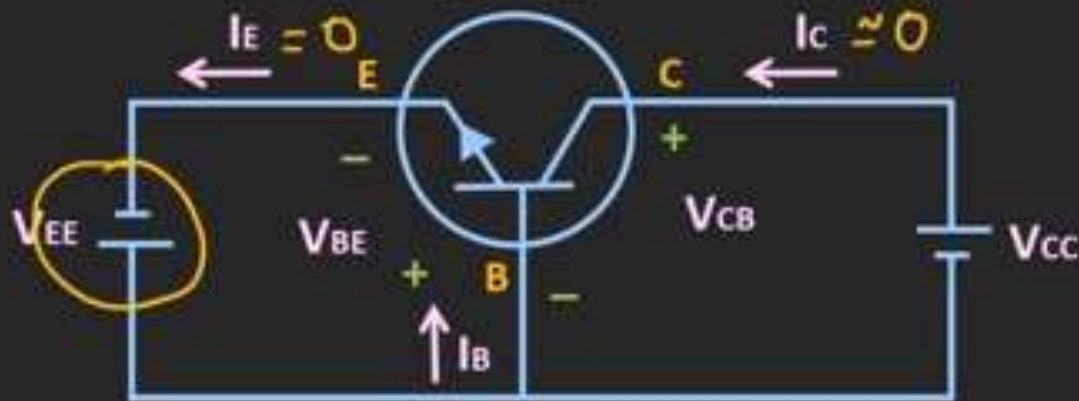


NPN Transistor

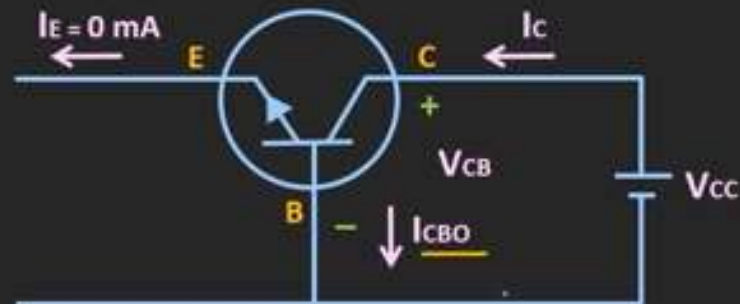

Common Base (CB) Configuration

NPN Transistor

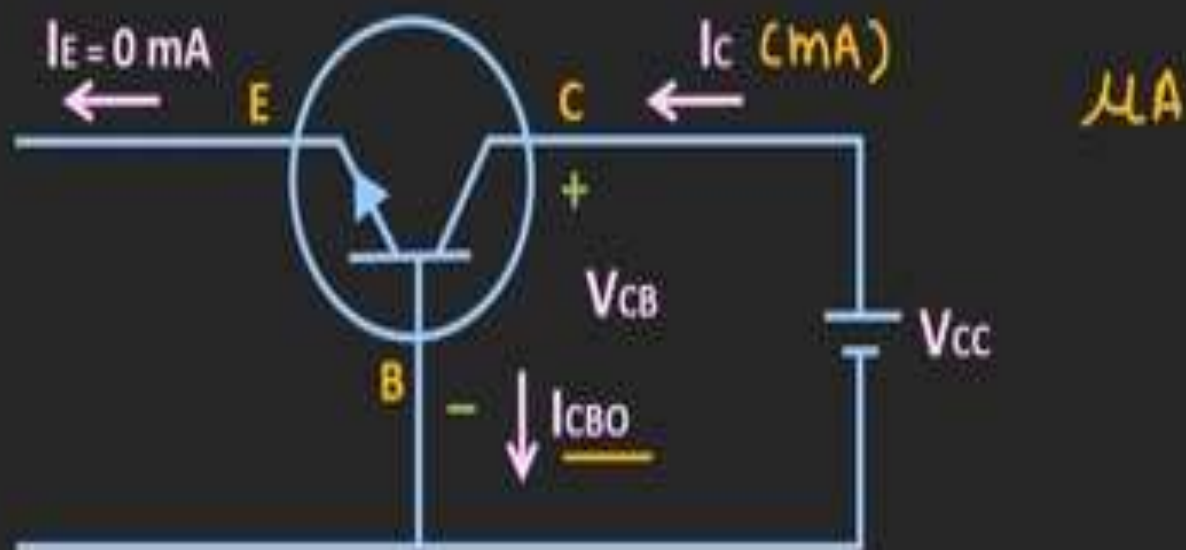

$$I_{CBO}$$


T ↑

$$I_{CT} = I_C + I_{CBO}$$

$$I_C = \alpha I_E + I_{CBO}$$

Common Base (CB) Configuration

Voltage Amplification

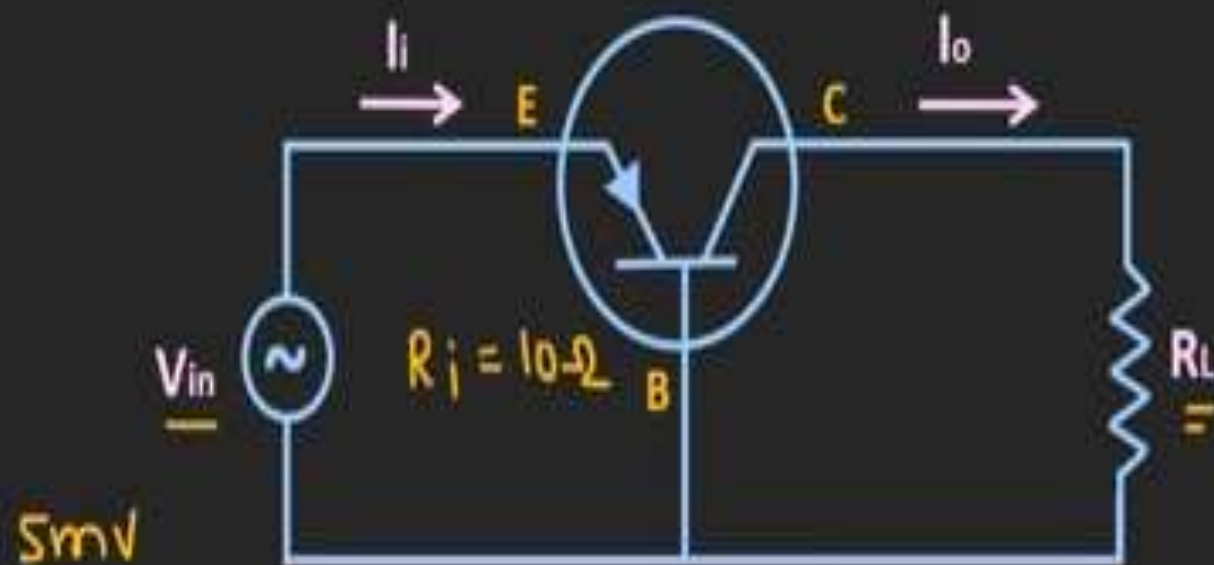

$$\alpha = 1$$

$$I_o = I_i$$


$$I_c = \alpha I_e$$

$$\Rightarrow I_c = I_e$$

$$I_i = \frac{5\text{mV}}{10\Omega} = 0.5\text{mA}$$

Common Base (CB) Configuration

Voltage Amplification

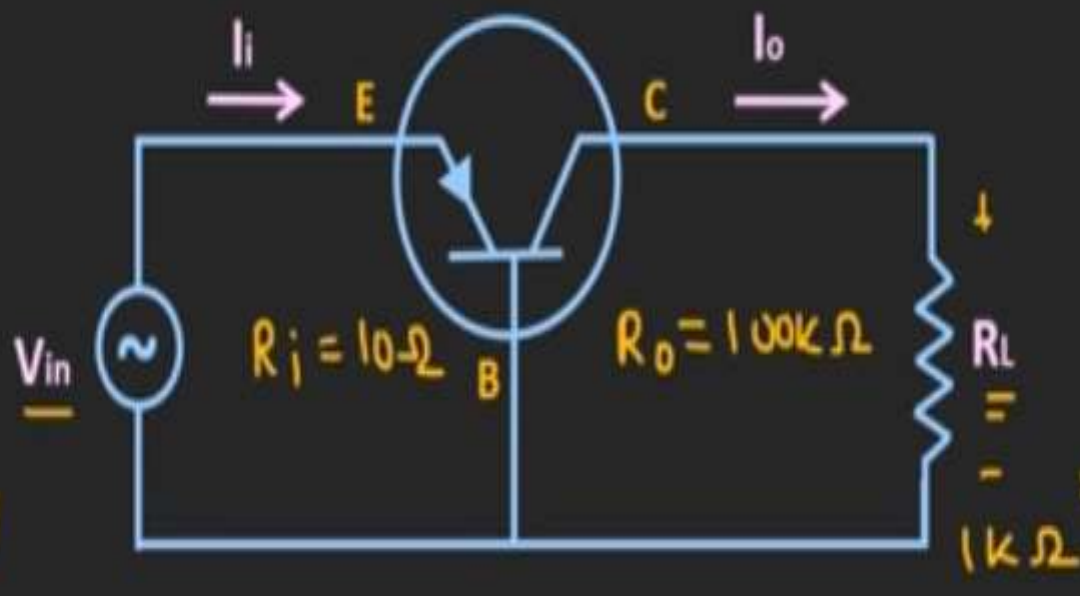

$$\frac{I_c}{I_e} < 1$$

$$\alpha = 1$$

$$I_o = I_i$$

$$I_c = \alpha I_e$$

$$\Rightarrow I_c = I_e$$

$$I_i = \frac{5\text{ mV}}{10\ \Omega} = 0.5\text{ mA}$$


$$\begin{aligned} V_o &= I_o R_L \\ &= 0.5\text{ mA} \times 1\text{ k}\Omega \\ &= 0.5\text{ V} = 500\text{ mV} \end{aligned}$$

$$\frac{100}{100}$$

$$\frac{5\text{ mV}}{10\ \Omega}$$


Common Base (CB) Configuration

Voltage Amplification

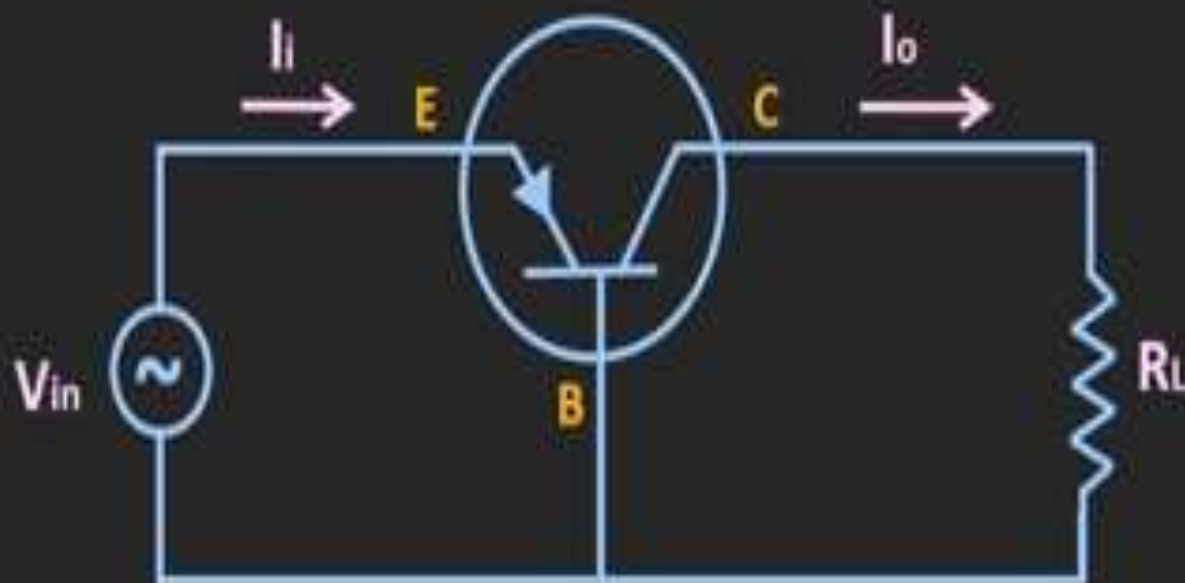


Transfer + Resistor = Transistor

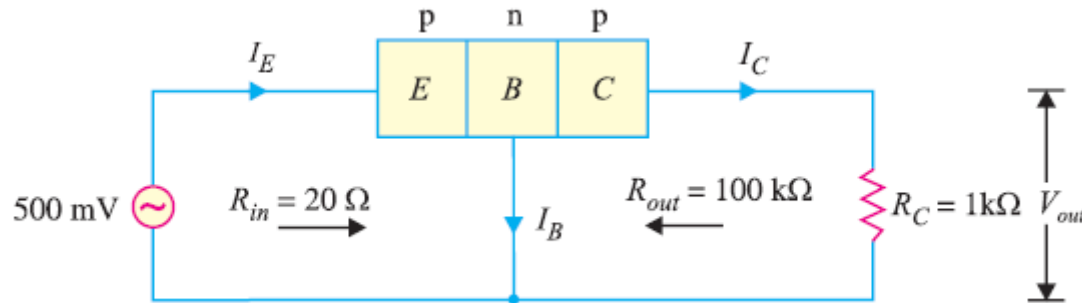A common base transistor amplifier has an input resistance of $20\ \Omega$ and output resistance of $100\ \text{k}\Omega$. The collector load is $1\ \text{k}\Omega$. If a signal of $500\ \text{mV}$ is applied between emitter and base, find the voltage amplification



<https://electronicspost.com/solved-problems-on-transistor/>

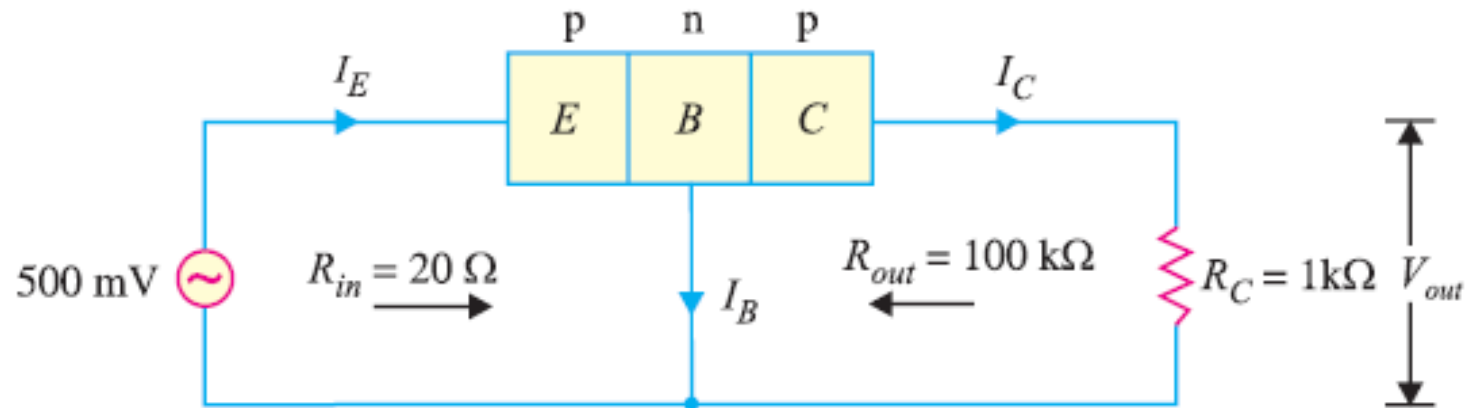A common base transistor amplifier has an input resistance of $20\ \Omega$ and output resistance of $100\ \text{k}\Omega$. The collector load is $1\ \text{k}\Omega$. If a signal of $500\ \text{mV}$ is applied between emitter and base, find the voltage amplification



Input current, $I_E = \frac{\text{Signal}}{R_{in}} = \frac{500\ \text{mV}}{20\ \Omega} = 25\ \text{mA}$. Since α_{ac} is nearly 1, output current, $I_C = I_E = 25\ \text{mA}$.

Output voltage, $V_{out} = I_C R_C = 25\ \text{mA} \times 1\ \text{k}\Omega = 25\ \text{V}$

\therefore Voltage amplification, $A_v = \frac{V_{out}}{\text{signal}} = \frac{25\ \text{V}}{500\ \text{mV}} = 50$

In a common base connection, current amplification factor is 0.9. If the emitter current is 1mA, determine the value of base current.

In a common base connection, current amplification factor is 0.9. If the emitter current is 1mA, determine the value of base current.

$$\text{Here, } \alpha = 0.9, \quad I_E = 1 \text{ mA}$$

Now

$$\alpha = \frac{I_C}{I_E}$$

or


$$I_C = \alpha I_E = 0.9 \times 1 = 0.9 \text{ mA}$$

Also

$$I_E = I_B + I_C$$

\therefore Base current, $I_B = I_E - I_C = 1 - 0.9 = 0.1 \text{ mA}$

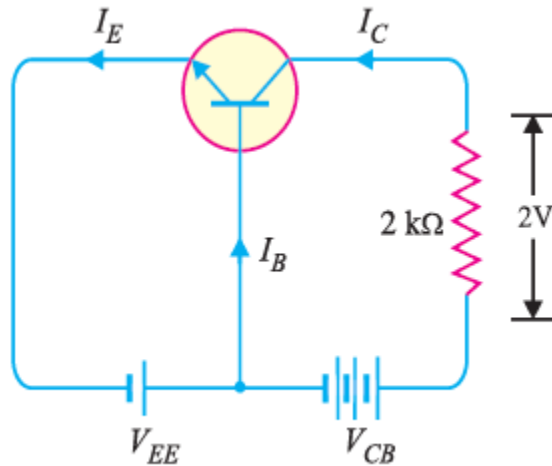In a common base connection, $\alpha = 0.95$. The voltage drop across $2\text{ k}\Omega$ resistance which is connected in the collector is 2 V . Find the base current.



\therefore
Now

$$I_C = 2\text{ V} / 2\text{ k}\Omega = 1\text{ mA}$$

$$\alpha = I_C / I_E$$

$$\therefore I_E = \frac{I_C}{\alpha} = \frac{1}{0.95} = 1.05\text{ mA}$$

Using the relation, $I_E = I_B + I_C$

$$\therefore I_B = I_E - I_C = 1.05 - 1$$

$$= \mathbf{0.05\text{ mA}}$$